

Special Problem 3.1 - 4

The diodes in the circuit below are **ideal**.

Find the **voltage across**, and **current through**, each ideal diode.

