

Special Problem 3.3-7

Using the *CVD* model, approximately determine the **current through**, and the **voltage across**, the **junction diode**.

