

Special Problem 3.6-2

Determine v_O as a function of v_I .

