

Special Problem 3.6-5

The diode in the circuit below is **ideal**.

Determine the **transfer function** for the limiter shown below.

In other words, determine V_o as a function of V_I .

