

Special Problem 4.11-2

The MOFET in the circuit below is a **depletion** type.

- 1) Determine the **drain current**.
- 2) Determine the **source voltage**.

