

Special Problem 4.3-1

Find the drain current I_D in the circuit below.

