

Special Problem 3.1-12

Both diodes in the circuit below are **ideal**.

Assume that the ideal diode D_1 is forward biased.

Assume that the ideal diode D_2 is reverse biased.

Determine the **voltage** across, and **current** through, **each** ideal diode

