

Special Problem 3.2-7

The junction diodes in the circuit below are **identical**, with ideality factor $n=1.0$ and scale current $I_s = 10^{-13}$ A.

A current of **6.0 mA** is flowing through resistor R_3 .

Determine the value of resistor R_4 in the circuit below.

