

### Special Problem 3.3-10

The circuit below includes one **small-signal** voltage source  $v_s$ .

The two junction diodes are **not** identical:  $D_1$  has ideality factor  $n=1.0$ , while  $D_2$  has an ideality factor  $n=2.0$ .

**I** have performed a **DC analysis** of this circuit (so you **don't** have to!), and have determined that:

1.  $D_1$  is forward biased, with  $I_{D1} = 10.0$  mA
2.  $D_2$  is forward biased, with  $I_{D2} = 1.0$  mA

Now, you perform the **small-signal analysis**, and:

1. Draw precisely the **small-signal circuit**, with **numeric** values for **each** resistor.
2. Determine (in terms of  $v_s$ ), the **small-signal voltages** across each diode (i.e.,  $V_{d1}$  and  $V_{d2}$ ).

