

Special Problem 3.3-6

The current source in the circuit below produces a **small signal** $i(t)$.

The junction diode has an ideality factor of $n = 1$.

Determine the **small-signal voltage** across the diode, in terms of small-signal current source $i(t)$.

