

Special Problem 3.3-7

Replace the junction diode with a **CVD model**, and then determine the approximate values the **current through**, and the **voltage across**, the **junction diode** in this circuit.

