

**Special Problem 3.4-2**

The zener diode in this circuit has a breakdown voltage of  $V_{ZK} = 10\text{ V}$ . Its dynamic resistance is so small that we can approximate it as zero.

Assuming that the zener diode is in breakdown, determine the current  $I_Z$ .

Is the assumption of breakdown correct? State why or why not.

