

Special Problem 3.4-7

The zener diode **breakdown voltage** is $V_{ZK} = 12.0 \text{ V}$.

Use the zener **CVD model** to analyze this circuit.

Estimate the voltage V_z across, and current I_z through, the zener diode.

