

**Special Problem 3.4 - 9**

The **zener** diode in the circuit below has a **breakdown voltage** of 20.0 V.

Use the **zener CVD model** to determine the **voltage** across and **current** through the **zener** diode (i.e.,  $V_z$  and  $I_z$ ).

