

Special Problem 3.5-8

The diode in the circuit below is **IDEAL**.

Determine the **transfer function** $v_o = f(v_I)$ of this circuit.

