

Special Problem 3.6-1

The diode in the circuit below has a Zener breakdown voltage of **18 volts**.

Determine the **transfer function** $v_o = f(v_i)$ for the diode **limiter** shown below, and plot this transfer function.

