

**Special Problem 3.6-2**

Determine  $v_O$  as a function of  $v_I$ .

