

Special Problem 3.6-4

The circuit below is a diode **limiter**.

Determine the **transfer function** (i.e., the function that describes v_o in terms of v_I) for this circuit.

