

Special Problem 4.11-1

The MOSFET in the circuit below is a **depletion** type.

Determine the **drain current** and **voltage drain to source**.

