

Special Problem 4.11-3

The current through resistor R_2 is $I_2 = 1.0 \text{ mA}$.

Determine the value of resistor R_3 .

