

Special Problem 4.2-1

The MOSFET in the circuit below has $K = 0.5 \text{ mA/V}^2$ and $V_T = -1.0 \text{ V}$.

First determine the **operating mode** of the MOSFET, and then determine the value of **current I** .

