

Special Problem 4.3-10

The **drain voltage** of the MOSFET below is $V_D = 2.0\text{ V}$.

Assume that the MOSFET in the circuit below is in the **saturation** mode.

1. Determine the value of **resistor R_1** .
2. Determine if the **assumption** was correct.

