

**Special Problem 4.3-12**

The current through resistor  $R_2$  is  $I_2 = 5.0 \text{ mA}$ .

Assume that the MOSFET in the circuit below is in the **triode** mode.

1. Determine the value of resistor  $R_3$ .
2. Determine if the **assumption** was correct.

