

Special Problem 4.3 - 5

For the circuit shown below, determine the value of resistor R_D .

