

Special Problem 4.3-6

The **gate voltage** of the transistor in the circuit below is **known** to be 7.0 V.

Assume that the MOSFET is in **saturation**.

- 1) Determine the value of the **resistor R** .
- 2) **Check** to see if the assumption is correct.

