

Special Problem 4.3-8

The drain voltage is known to be 4.0 V.

Determine the value of the MOSFET threshold voltage V_t .

