

**Special Problem 4.3-9**

Assume that the MOSFET in the circuit below is in **triode** mode.

The current through resistor  $R_1$  is **2mA**.

- 1) Find the value of **resistor  $R$** .
- 2) Determine if the **assumption** is correct.

