

Special Problem 5.4-1

Assume the BJT in the circuit below is in **active** mode.

1. Using this assumption, determine the emitter, base, and collector **currents**, as well as the emitter, base and collector **voltages**.

2. Determine if the **active assumption** was correct.

