

**Special Problem 5.4-3**

Assume that the BJT is in **saturation** mode.

Find then the **base, emitter, and collector currents**.

Determine whether the saturation assumption was correct.

