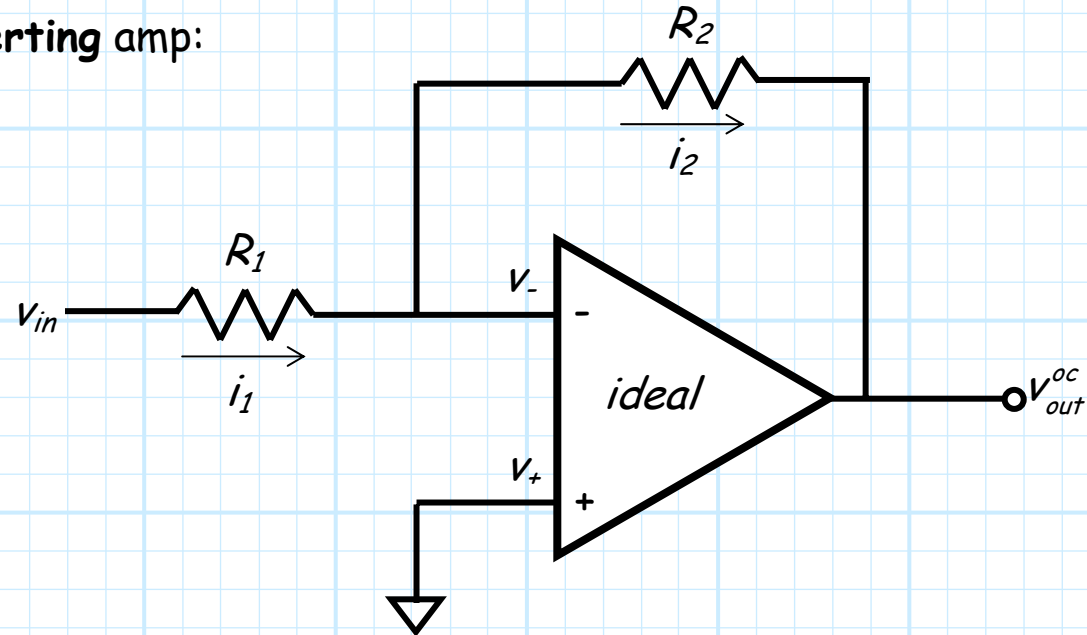


Feedback Stability

Recall that for the **inverting amp**:



we have the **feed-forward** equation:

$$v_{out}^{oc} = -A_{op} v_{-}$$

and the **feed-back** equation:

$$v_{-} = \frac{R_2 v_{in} + R_1 v_{out}^{oc}}{R_1 + R_2}$$

Nothing more fun than calculus!

Taking **derivatives** of these equations, we find that:

$$\frac{\partial v_{out}^{oc}}{\partial v_-} = \frac{\partial(-A_{op} v_-)}{\partial v_-} = -A_{op}$$

and:

$$\frac{\partial v_-}{\partial v_{out}^{oc}} = \frac{\partial}{\partial v_{out}^{oc}} \left(\frac{R_2 v_{in} + R_1 v_{out}^{oc}}{R_1 + R_2} \right) = \frac{R_1}{R_1 + R_2}$$

These derivatives are **very** important in determining the **stability** of the feedback amplifier.

Feed-forward

To see this, consider what happens when, for some reason, v_- **changes** some small value Δv_- from its nominal value of $v_- = 0$.

The **output** voltage will then likewise change by a value Δv_{out}^{oc} :

$$\Delta v_{out}^{oc} \approx \left(\frac{\partial v_{out}^{oc}}{\partial v_-} \right) \Delta v_- = -A_{op} \Delta v_1$$

Note if Δv_- is **positive**, then Δv_{out}^{oc} will be **negative**—an **increase** in v_- leads to a **decrease** in v_{out}^{oc} .

This describes the **feed-forward** portion of the "loop."


Feed-back

The feed-back equation states that a small change in the **output** voltage (i.e., Δv_{out}^{oc}), will likewise result in a small change in v_- :

$$\Delta v_- \approx \left(\frac{\partial v_-}{\partial v_{out}^{oc}} \right) \Delta v_{out}^{oc} = \left(\frac{R_1}{R_1 + R_2} \right) \Delta v_{out}^{oc}$$

Note in this case, a **decreasing** output voltage will result in a **decreasing** inverting terminal voltage v_- .

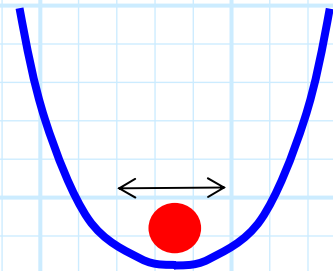Thus, if the inverting terminal voltage tries to **increase** from its correct value of $v_- = 0$, the control loop will react by **decreasing** the voltage v_- —essentially **counteracting** the initial change!



Negative feedback-in this case it's a good thing!

Note that the **loop product**:


$$\frac{\partial V_{out}^{oc}}{\partial V_-} \frac{\partial V_-}{\partial V_{out}^{oc}} = -A_{op} \left(\frac{R_1}{R_1 + R_2} \right)$$

is a **negative** value; we refer to this case as **negative feedback**.

Negative feedback keeps the inverting voltage in place (i.e., $v_- = 0$)—it “enforces” the concept of the virtual ground!

Let's try some positive feedback

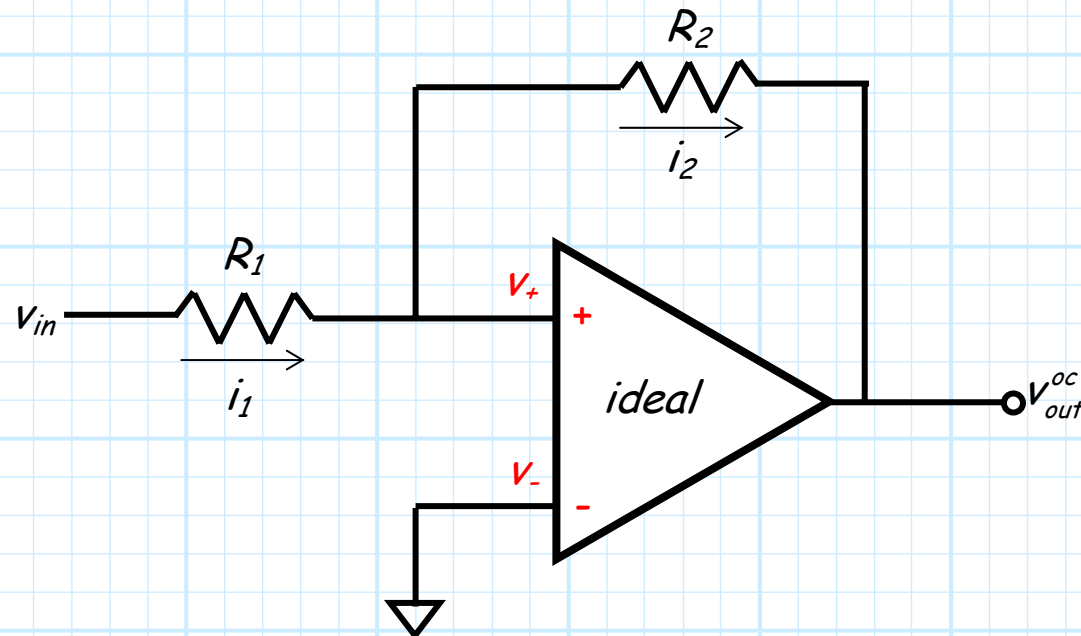Contrast this behavior with that of the following circuit:



Q: *Isn't this precisely the **same** circuit as before?*

A: NO!

Note that the feedback resistor is now connected to the **non-inverting** terminal, and the **inverting** terminal is now grounded.

Positive derivatives!

The feed-forward equations for this circuit are thus:

$$v_{out}^{oc} = A_{op} v_+$$

And so:

$$\frac{\partial v_{out}^{oc}}{\partial v_+} = \frac{\partial (A_{op} v_+)}{\partial v_+} = A_{op}$$


while the feed-back equations are:

$$v_+ = \frac{R_2 v_{in} + R_1 v_{out}^{oc}}{R_1 + R_2}$$


and:

$$\frac{\partial v_+}{\partial v_{out}^{oc}} = \frac{\partial}{\partial v_{out}^{oc}} \left(\frac{R_2 v_{in} + R_1 v_{out}^{oc}}{R_1 + R_2} \right) = \frac{R_1}{R_1 + R_2}$$

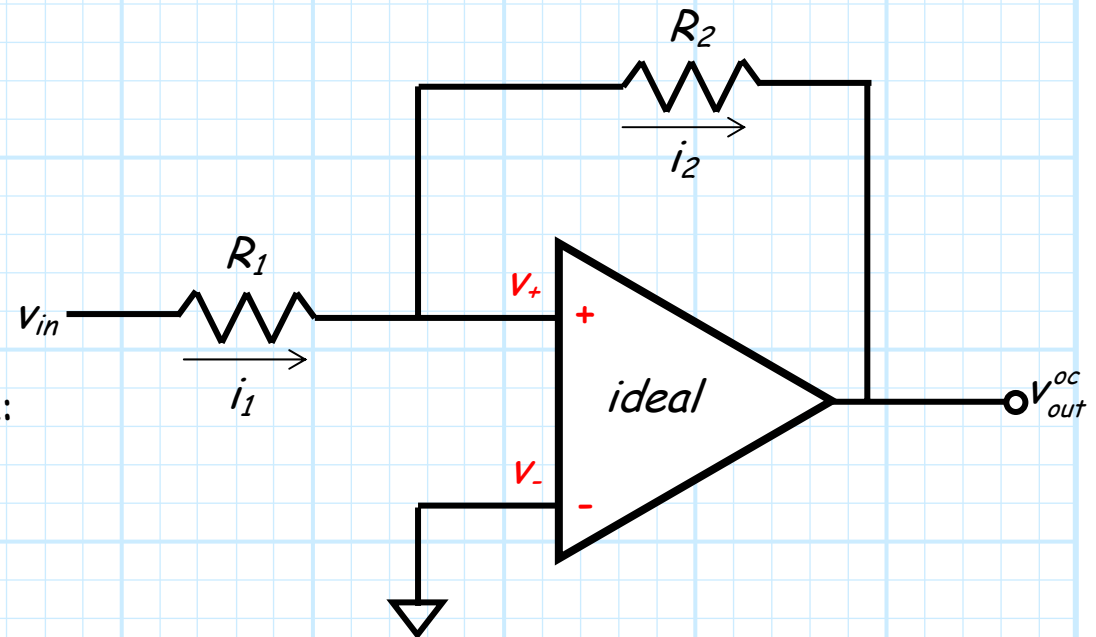Note in this case, **both derivatives are positive.**



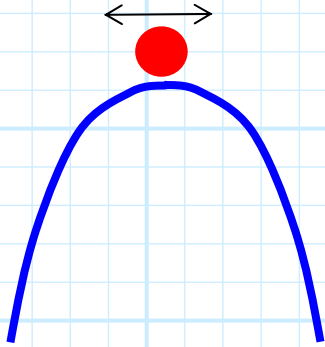Positive feedback-in this case it's a bad thing!



This means that an **increase** in v_+ will lead to an **increase** in v_{out}^{oc} . The problem is that the feedback will react by **increasing** v_+ even more—the error is **not** corrected, it is instead **reinforced**!

The result is that the output voltage will be sent to $v_{out}^{oc} = \infty$ or $v_{out}^{oc} = -\infty$ (i.e., the amplifier will **saturate**).

Note that the **loop product** for this case is **positive**:

$$\frac{\partial v_{out}^{oc}}{\partial v_+} \frac{\partial v_+}{\partial v_{out}^{oc}} = A_{op} \left(\frac{R_1}{R_1 + R_2} \right)$$

Thus, we refer to this case as **positive feedback**.

→ Positive feedback typically leads to amplifier instability!

As a result, we find that the **feed-back** portion of an op-amp circuit almost always is connected to its **inverting (-)** terminal!