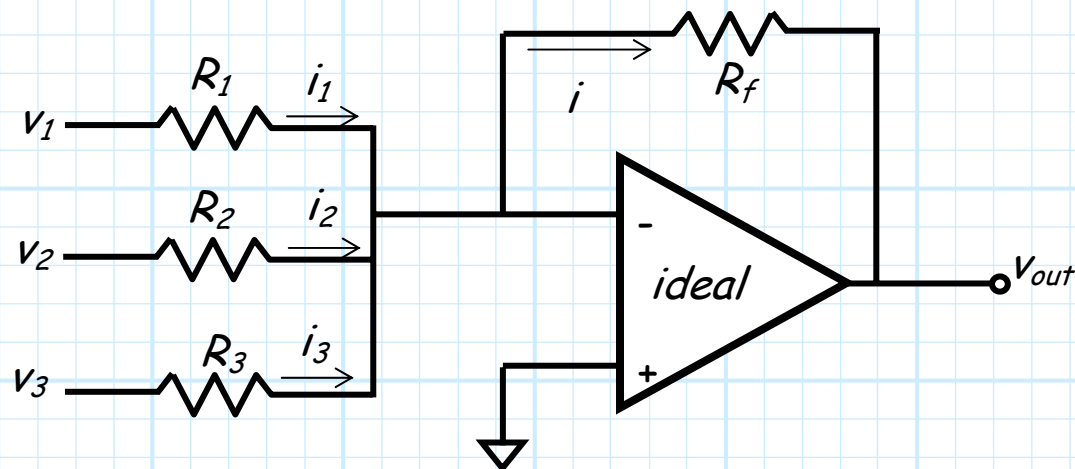


# The Weighted Summer

Consider an inverting amplifier with **multiple** inputs!



From **KCL**, we can conclude that the currents are related as:

$$i = i_1 + i_2 + i_3$$

and because of **virtual ground** ( $i_- = i_+ = 0$ ), we can conclude from **Ohm's Law**:

$$i_1 = \frac{V_1 - V_-}{R_1} = \frac{V_1}{R_1}$$

$$i_2 = \frac{V_2 - V_-}{R_2} = \frac{V_2}{R_2}$$

$$i_3 = \frac{V_3 - V_-}{R_3} = \frac{V_3}{R_3}$$


## The output voltage

Likewise:

$$i = \frac{V_- - V_{out}}{R_f} = \frac{-V_{out}}{R_f}$$

Inserting these results into the initial KCL expression:
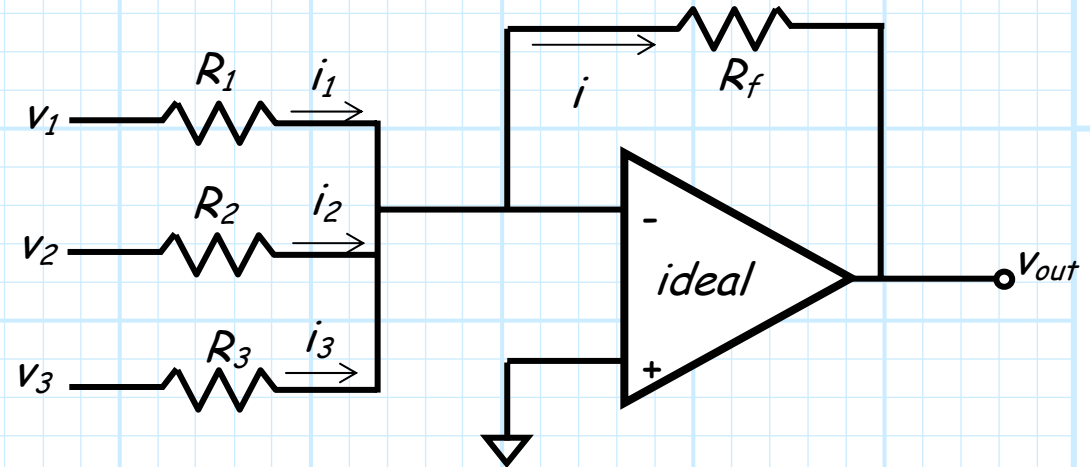
$$\frac{-V_{out}}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$



Now, we sprinkle on some algebraic pixie dust, and find the output voltage:

$$V_{out} = -\frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} V_3$$

The output is thus a weighted summation of each of the input signals!

We therefore refer to this circuit as the **weighted summer**.

## How to combine signals

Note that if  $R_f = R_1 = R_2 = R_3$ , the output is an **unweighted summer**:

$$v_{out}(t) = - (v_1(t) + v_2(t) + v_3(t))$$

For example, if:

$$v_1(t) = 2.0 \cos(2\pi t + \pi)$$

$$v_2(t) = 1.0 \cos(2\pi t + \pi/3)$$

$$v_3(t) = 1.5 \cos(2\pi t - \pi/4)$$

then:

$$v_{out}(t) = -2.0 \cos(2\pi t + \pi) - 1.0 \cos(2\pi t + \pi/3) - 1.5 \cos(2\pi t - \pi/4)$$

The summer is a method for **combining** several signals!