

**Special Problem 2.3-1**

Find an expression for  $v_{out}$  in terms of  $v_{in}$  for the circuit shown below.

