

Special Problem 2.3-5

Determine **output voltage** $v_{out}(t)$ in terms of input voltage $v_{in}(t)$.

