

**Special Problem 2.3-6**

For the following circuit, **determine**  $v_{out}$  in terms of  $v_{in}$ .

