

Special Problem 2.3-7

Determine the open-circuit voltage gain (v_{out}/v_{in}) of this amplifier.

