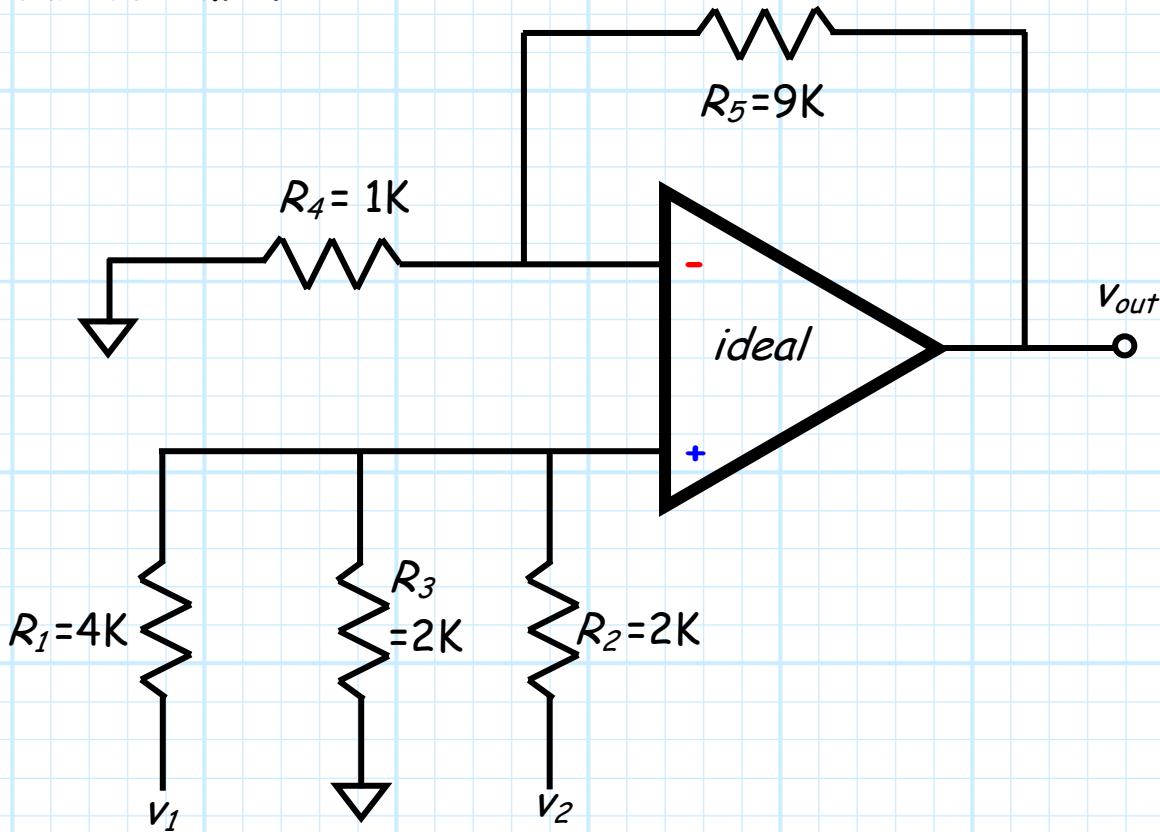


### Special Problem 2.4-2



For the circuit above, determine:

1. output  $v_{out}$  in terms of inputs  $v_1$  and  $v_2$ .
2. both the **differential** and **common-mode** gains of this amplifier.
3. the **CMRR**.