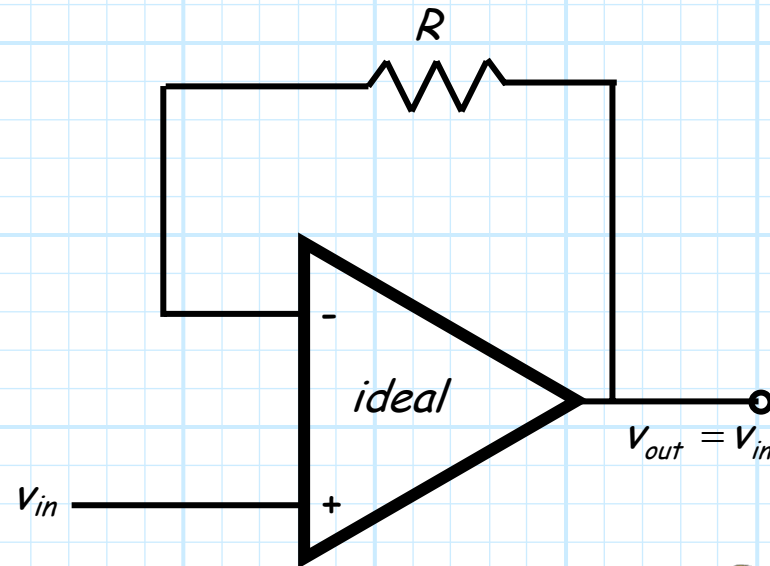



The Voltage Follower

The **voltage follower** has a open-circuit voltage gain $A_{vo} = 1$ —with the result that $V_{out} = V_{in}$!



Q: Pfft! The output voltage is equal to the input voltage?!

Why even bother?

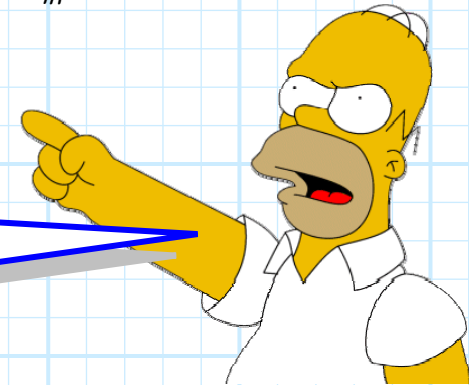

A: To see **why** the voltage follower is **important**, consider the following example.


What a great amp...

Say **you** have toiled for hours to design and build the following **audio amplifier**:

$$A_{vo} = -200 \text{ (midband)}$$

$$R_{out} = 1 \text{ K}$$

$$R_i = 370 \text{ } \Omega$$

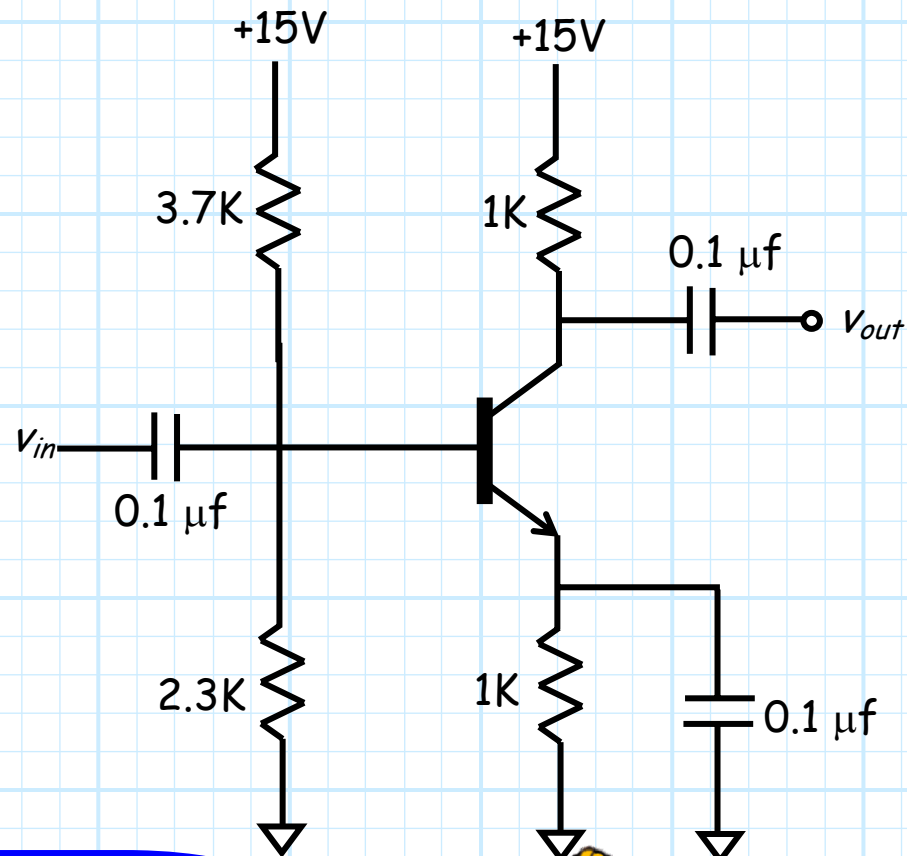


Q: $A_{vo} = -200$! With this much gain we'll be shakin the windows—right?



...or, maybe not

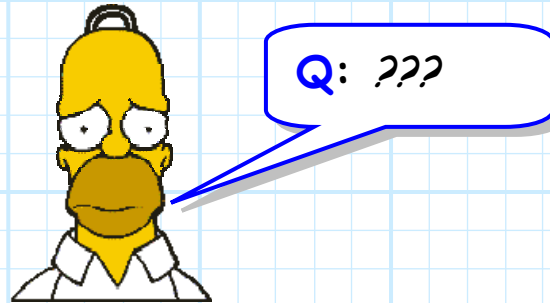A: Actually, if we connected this amplifier **directly** to a speaker, **nothing** would happen—**silence!**




A: The reason for this is that the **resistance** of most **speakers** is **very small** ($4\ \Omega$ - $8\ \Omega$).



What's the problem then?

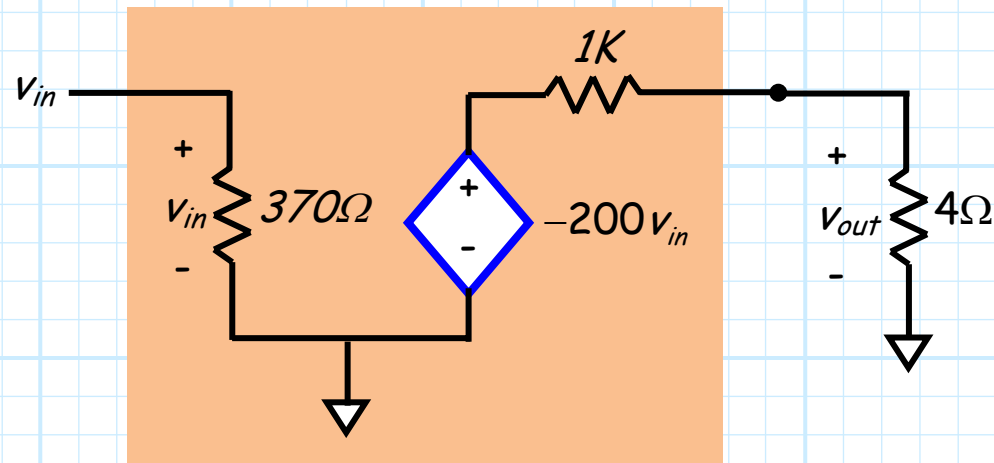We can use the linear equivalent **circuit model** of the audio amplifier to **analyze** the result:



$$V_{out} = -200V_{in} \left(\frac{4}{4 + 1000} \right) = -0.8V_{in}$$

The **output** of this amplifier is even **smaller** than its **input**!

The **problem**, of course, is **not** that the open-circuit voltage **gain** is too small—after all, it's -200!


The output resistance is just too large!

The **problem** is that the amplifier **output resistance** ($R_{out} = 377\Omega$) is much larger than the **load resistance** $R_L = 4\Omega$.

Therefore, we have **tremendous loss** due to the resulting **voltage divider**:


$$\frac{4}{4 + 1000} \approx 0.004$$

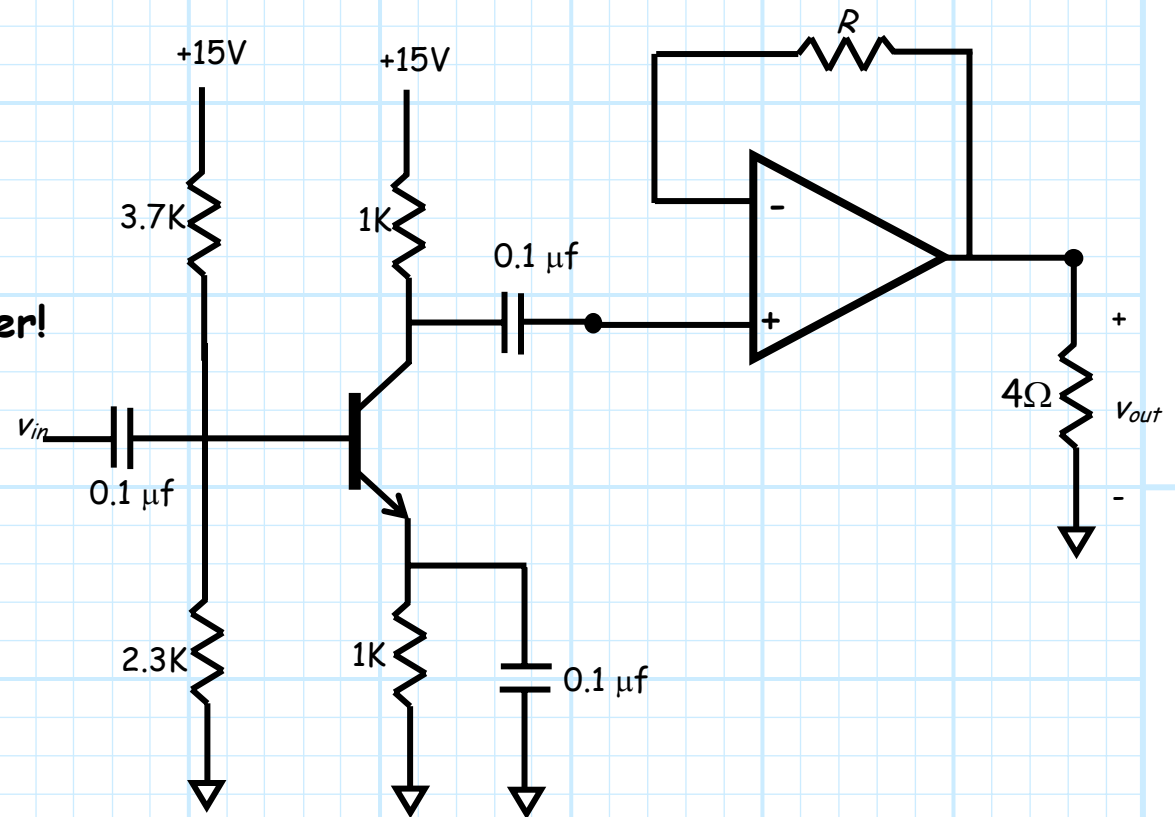There is a solution to this problem—use a voltage follower!



The voltage follower to the rescue!

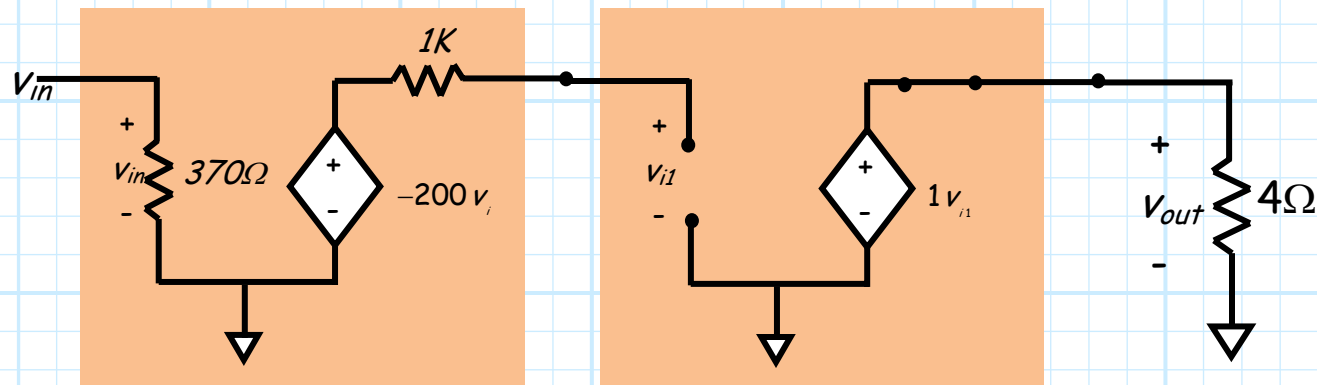Let's again use the **linear equivalent model** to analyze this circuit and find the output voltage v_{out} .



$$v_{out} = -200 v_{in} \left(\frac{\infty}{1000 + \infty} \right) 1 \left(\frac{4}{0 + 4} \right) = -200 v_{in}$$

We've got back our **gain!**

The voltage follower: a useful buffer

Note:

1. **Instead of 4Ω , the audio amp "sees" a load of ∞ , the input resistance of the voltage follower—this is **ideal!****
2. **Instead of 377Ω , the speaker "sees" a source resistance of 0, the output resistance of the voltage follower—this too is **ideal!****

Remember, there are **three** characterizing parameters of an amplifier—open circuit voltage gain is just **one** of those three!

The input and output impedance of the voltage follower make it an excellent "**buffer**" between two circuits!