

2.3 The Non-Inverting Configuration

Reading Assignment: *pp.*

Another standard op-amp circuit configuration is the non-inverting configuration.

HO: THE NON-INVERTING CONFIGURATION

An important non-inverting circuit is the voltage follower.

HO: THE VOLTAGE FOLLOWER