

2.4 Difference Amplifiers

Reading Assignment:

Op-amp circuits often have more than one inputs; the best way to analyze these circuits is with **superposition!**


HO: SUPERPOSITION AND OP-AMP CIRCUITS

Many two input op-amp circuits are differential amplifiers. These circuits should exhibit a large **common-mode rejection ratio!**

HO: DIFFERENTIAL AND COMMON MODE GAIN

Superposition and Op-Amp Circuits

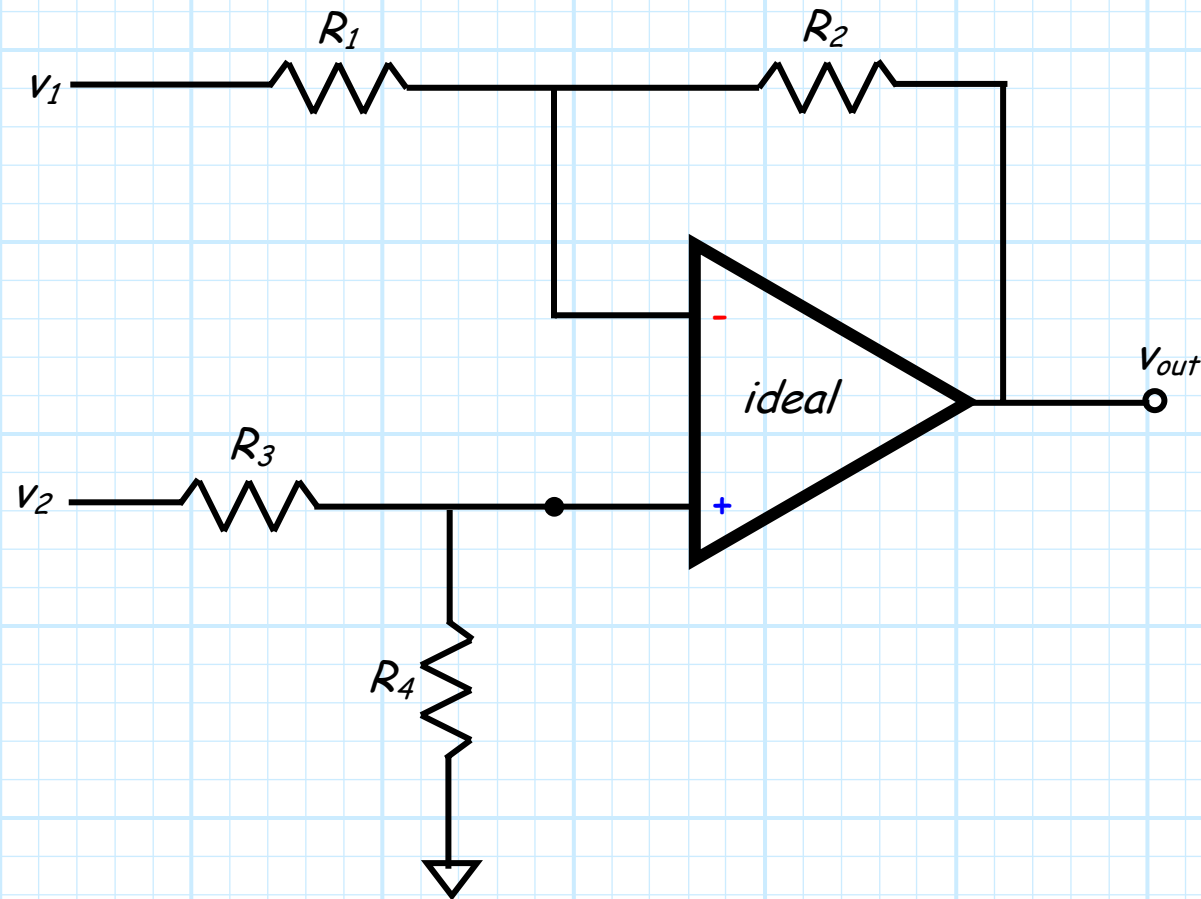
Consider **this** op-amp circuit, with two input voltages (v_1 and v_2):



Apply superposition

The **easiest** way to analyze this circuit is to apply **superposition**! Recall that op-amp circuits are **linear**, so superposition applies.

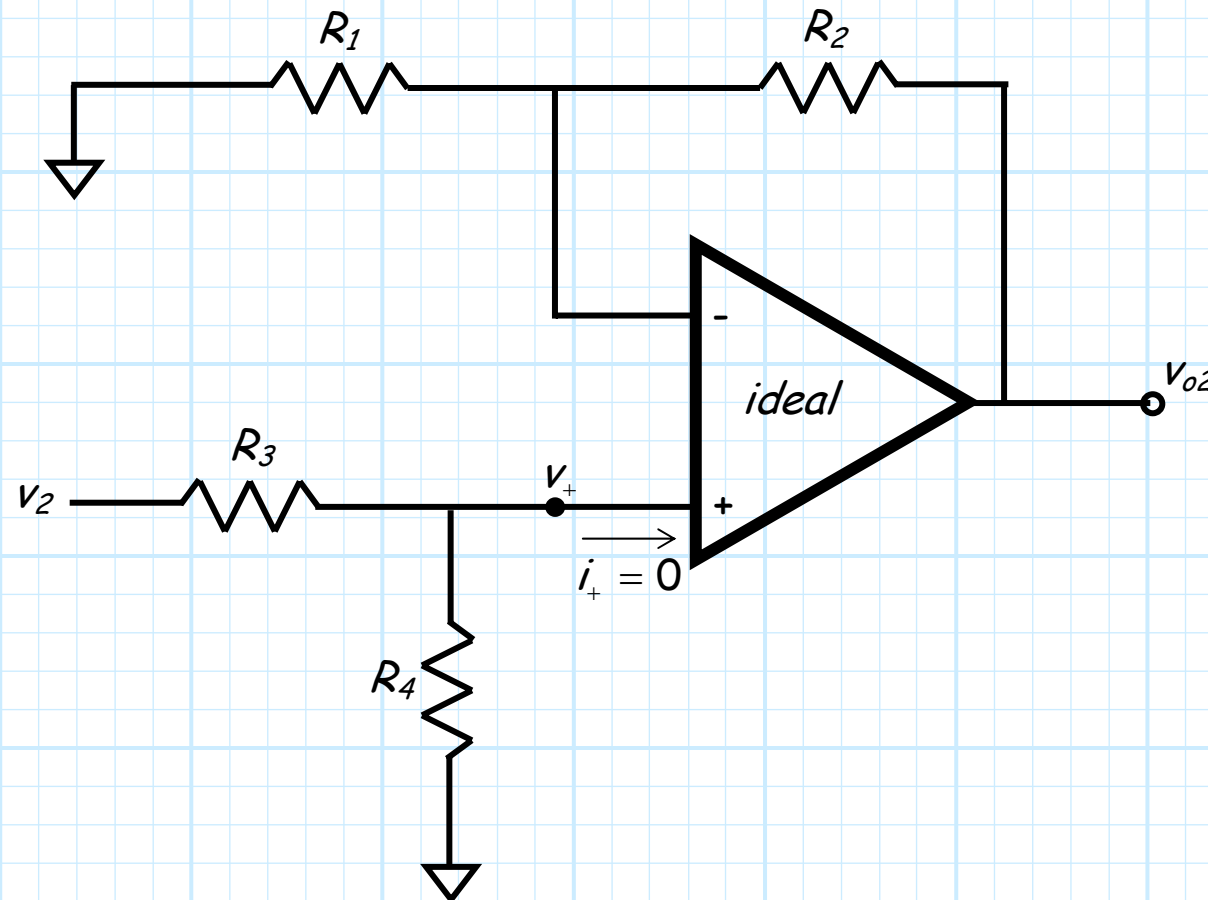Our **first step** is to set all sources to zero, **except** v_2 —in other words, set $v_1 = 0$ (connect it to ground potential):



$$\underline{v_1 = 0}$$

Since the current into the non-inverting input of the op-amp is zero ($i_+ = 0$), it is evident that:


$$v_+ = \frac{R_4}{R_3 + R_4} v_2$$

Likewise, the remainder of the circuit is simply the **non-inverting amplifier**, where:

$$v_{o2} = \left(1 + \frac{R_2}{R_1}\right) v_+$$


Combining these two equations, we get:
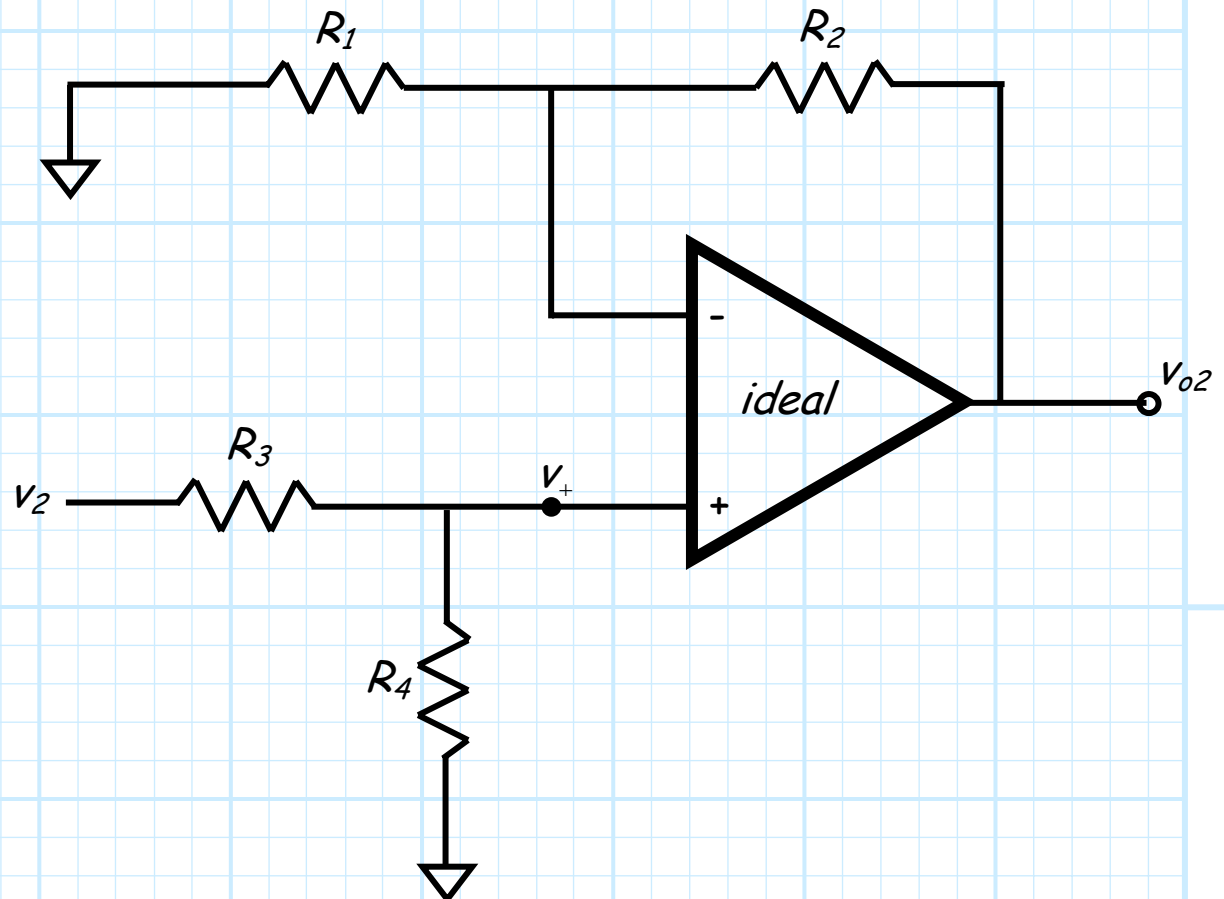
$$v_{o2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) v_2$$



$$\underline{v_2 = 0}$$

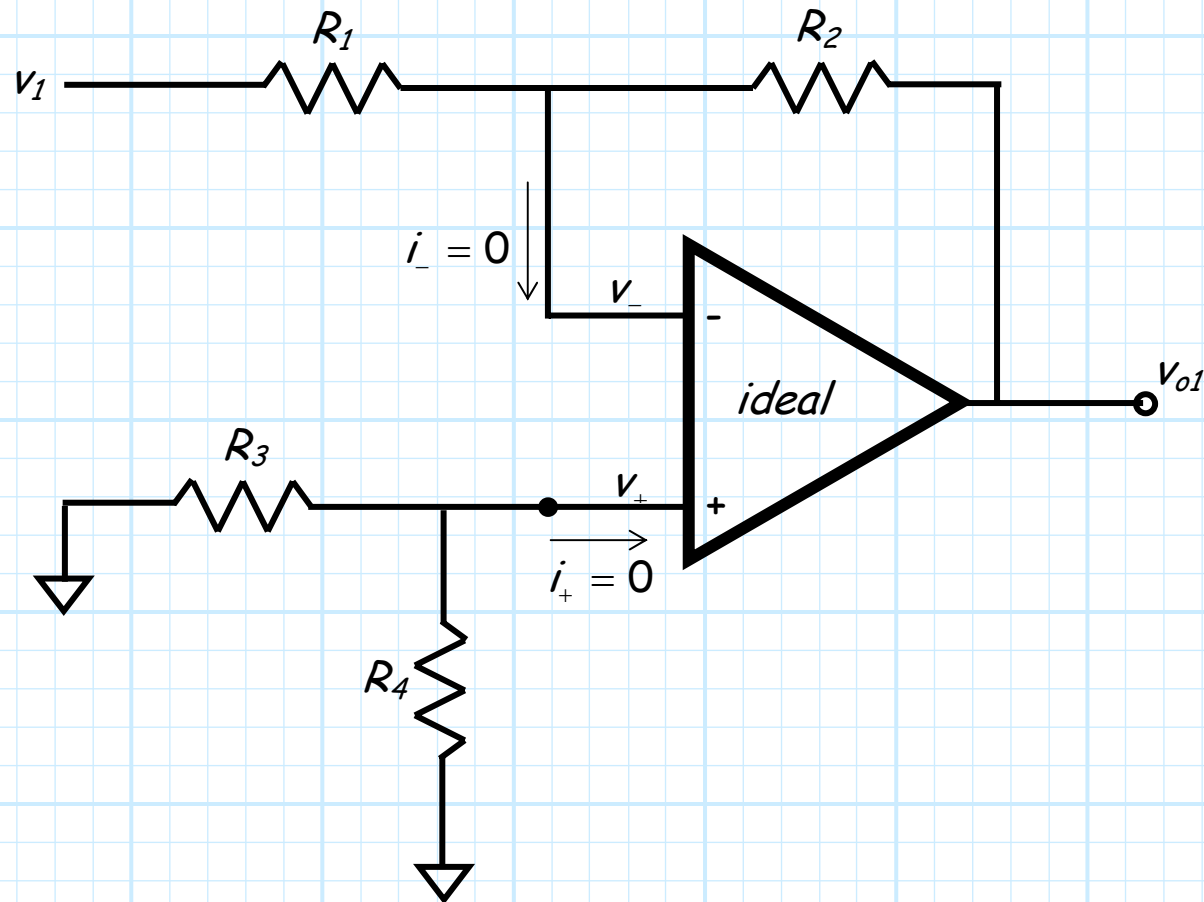
Now for the **second step**. Turn off all sources except v_1 —in other words set $v_2 = 0$:



An inverting amp

It is evident that since the current into the non-inverting terminal of the op-amp is **zero**, the voltage v_+ is likewise **zero**.

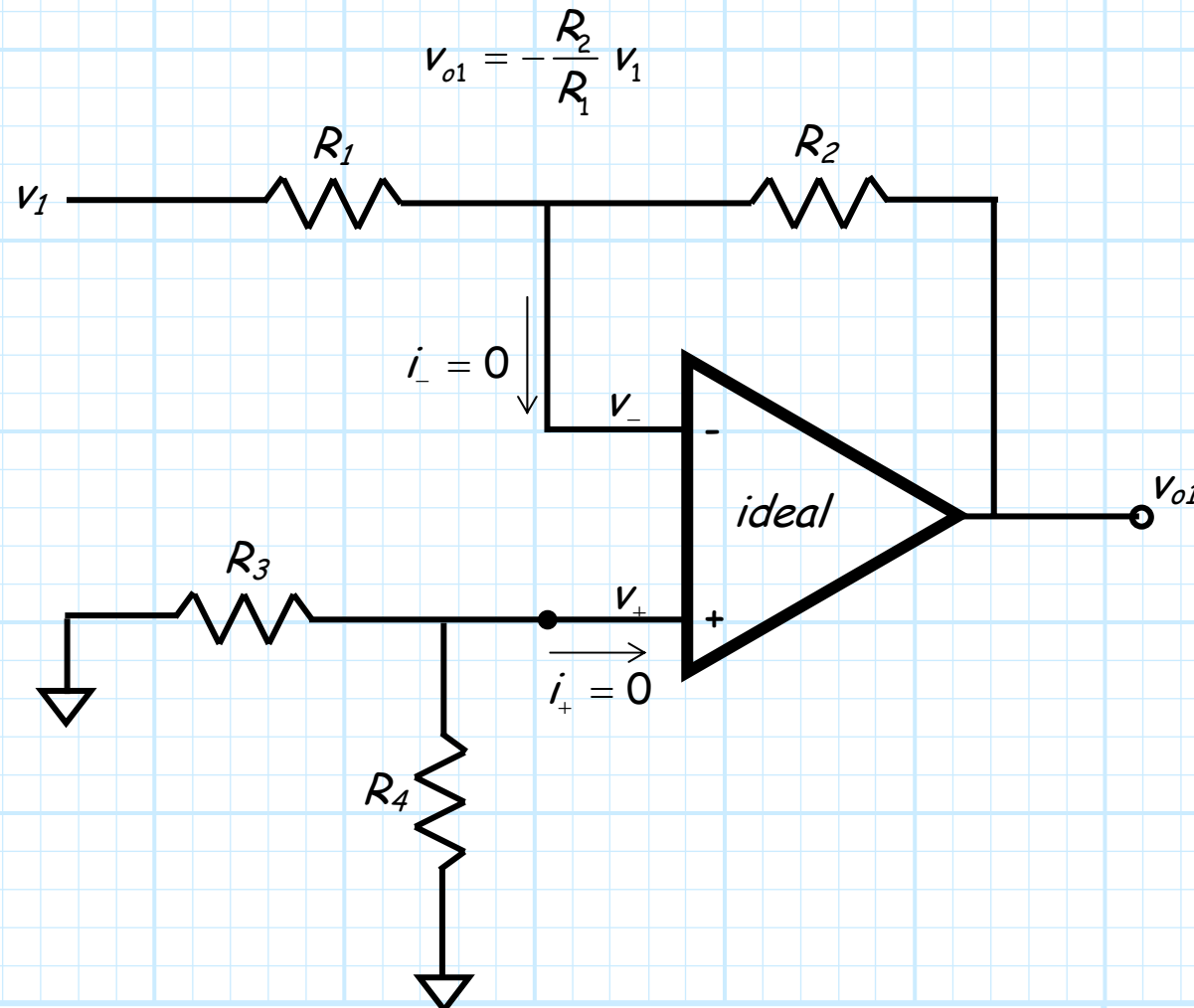Thus, the circuit above is simply an **inverting amplifier**, where:




And the result

There are **no** more sources in this circuit, so that we can conclude from **superposition** that the output voltage is the sum of our two, single-source solutions:


$$V_{out} = V_{o1} + V_{o2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_2 - \left(\frac{R_2}{R_1}\right) V_1$$

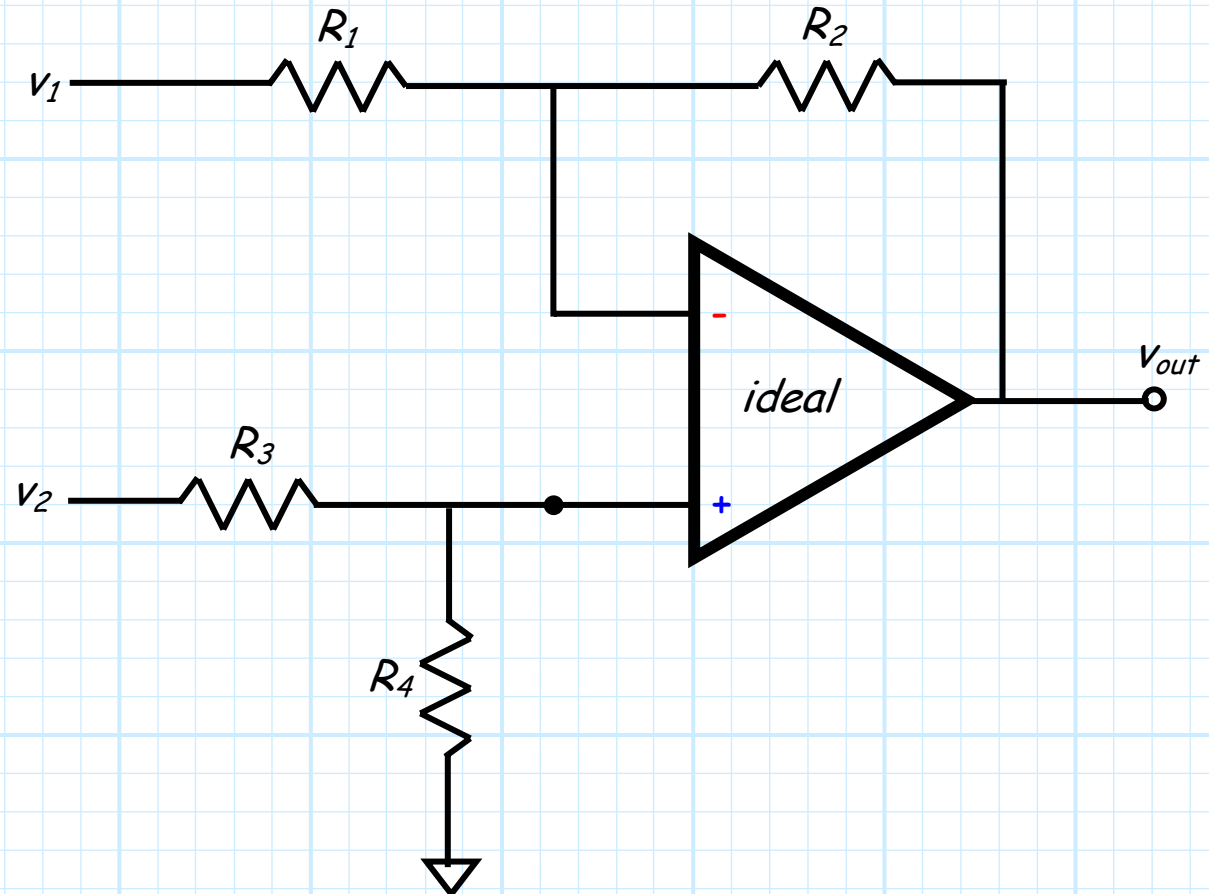Note this circuit is effectively a **weighted difference amplifier**.



Differential and Common-Mode Gain

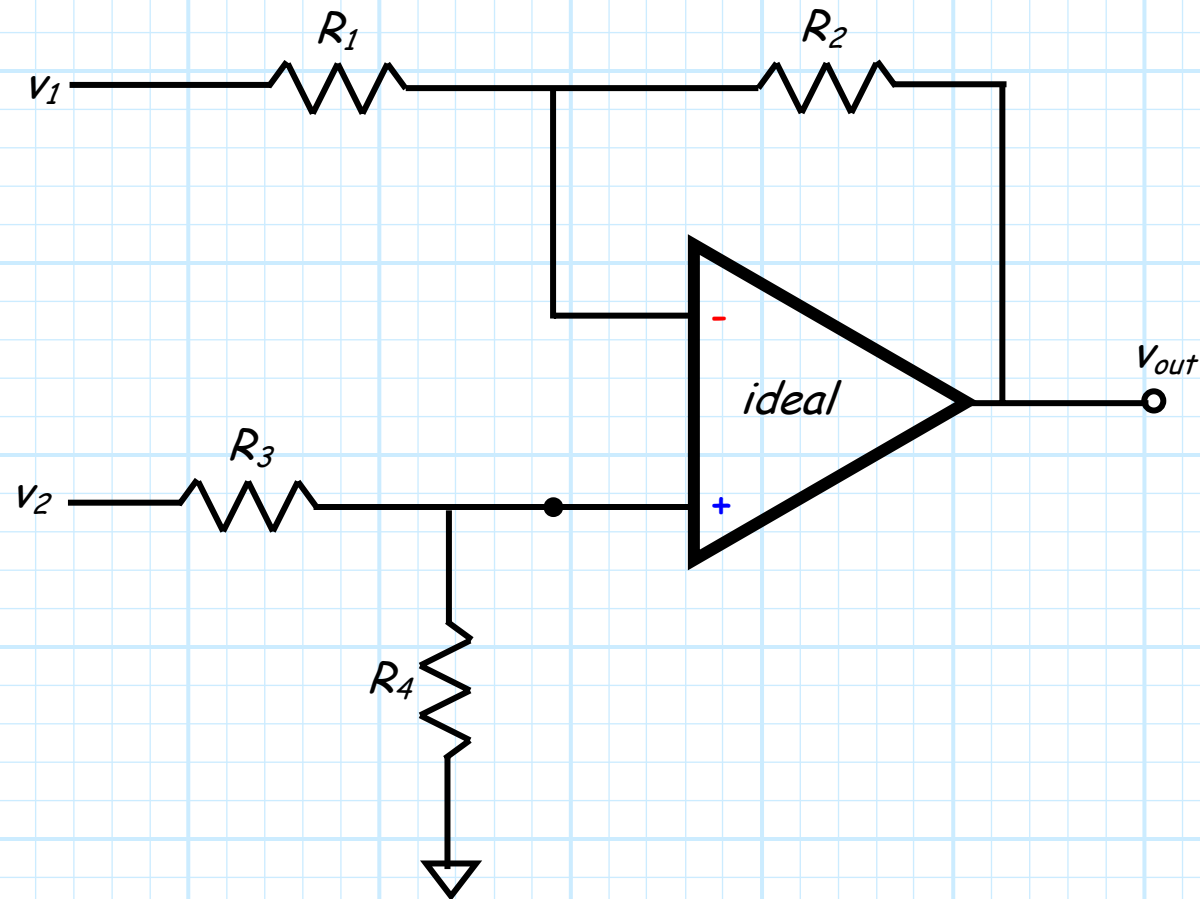Recall that in a previous handout, we analyzed **this** circuit:



Common mode and differential mode

We found that the output is related to the inputs as:

$$v_{out} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) v_2 - \left(\frac{R_2}{R_1}\right) v_1$$

This circuit is a **weighted difference amplifier**, and typically, it is expressed in terms of its **differential gain** A_d and **common-mode gain** A_{cm} .

To understand what these gains mean, we must first define the **difference signal** $v_d(t)$ and **common-mode signal** $v_{cm}(t)$ of two inputs $v_1(t)$ and $v_2(t)$.

Definitions

The **difference**, as we might expect, is defined as:

$$v_d(t) \doteq v_2(t) - v_1(t)$$

whereas the **common-mode** signal is simply the **average** of the two inputs:

$$v_{cm}(t) \doteq \frac{v_2(t) + v_1(t)}{2}$$

Using these definitions, we can express the two input signals as:

$$v_2(t) = v_{cm}(t) + \frac{v_d(t)}{2}$$

$$v_1(t) = v_{cm}(t) - \frac{v_d(t)}{2}$$

A new way to express the output

Thus, the differential signal $v_d(t)$ and the common-mode signal $v_{cm}(t)$ provide another way to **completely** specify input signals $v_1(t)$ and $v_2(t)$ —if you know $v_d(t)$ and $v_{cm}(t)$, you know $v_1(t)$ and $v_2(t)$.

Moreover, we can express the behavior of our **differential amplifier** in terms of $v_d(t)$ and $v_{cm}(t)$. Inserting these functions into the expression of the amplifier output $v_o(t)$, we find:

$$\begin{aligned}
 v_{out} &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) v_2 - \left(\frac{R_2}{R_1}\right) v_1 \\
 &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) \left(v_{cm}(t) + \frac{v_d(t)}{2}\right) - \left(\frac{R_2}{R_1}\right) \left(v_{cm}(t) - \frac{v_d(t)}{2}\right) \\
 &= \frac{1}{2} \left[\left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) + \left(\frac{R_2}{R_1}\right) \right] v_d(t) \\
 &\quad + \left[\left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \left(\frac{R_2}{R_1}\right) \right] v_{cm}(t) \\
 &= \frac{R_1 R_4 + R_2 R_3 + 2R_2 R_4}{2R_1 (R_3 + R_4)} v_d(t) + \frac{R_1 R_4 - R_2 R_3}{R_1 (R_3 + R_4)} v_{cm}(t)
 \end{aligned}$$

A more "common" form

Thus, we now have an expression for the **open-circuit** output in the form:

$$v_{out}(t) = A_d v_d(t) + A_{cm} v_{cm}(t)$$

where:

$A_d \doteq$ differential gain

$A_{cm} \doteq$ common-mode gain

Difference amplifiers should have no common-mode gain

Note that each of these gains are **open-circuit voltage** gains.

- * An **ideal** differential amplifier has **zero** common-mode gain (i.e., $A_{cm}=0$)!
- * In other words, the output of an **ideal** differential amplifier is **independent** of the **common-mode** (i.e., average) of the two input signals.
- * We refer to this characteristic as **common-mode suppression**.

Typically, **real** differential amplifiers exhibit **small**, but non-zero common mode gain.

Common-Mode Rejection ratio

The **Common-Mode Rejection Ratio (CMRR)** is therefore used to indicate the **quality** of a differential amplifier:

$$\text{CMRR} = 10 \log_{10} \frac{|A_d|^2}{|A_{cm}|^2} \quad (\text{dB})$$

Note the CMRR of a **good** differential amplifier is very **large** (e.g., > 40 dB).

For our **example** circuit, we find that the differential and common-mode gain are:

$$A_d = \frac{R_1 R_4 + R_2 R_3 + 2R_2 R_4}{2R_1 (R_3 + R_4)}$$

$$A_{cm} = \frac{R_1 R_4 - R_2 R_3}{R_1 (R_3 + R_4)}$$

Common-mode gain depends on design

The ratio of these two gains is thus:

$$\frac{A_d}{A_{cm}} = \left(\frac{R_1 R_4 + R_2 R_3 + 2R_2 R_4}{2R_1 (R_3 + R_4)} \right) \left(\frac{R_1 R_4 - R_2 R_3}{R_1 (R_3 + R_4)} \right)^{-1}$$

$$= \frac{1}{2} \frac{R_1 R_4 + R_2 R_3 + 2R_2 R_4}{R_1 R_4 - R_2 R_3}$$

and therefore CMRR is:

$$\text{CMRR} = 10 \log_{10} \left| \frac{1}{2} \frac{R_1 R_4 + R_2 R_3 + 2R_2 R_4}{R_1 R_4 - R_2 R_3} \right|^2 \quad (\text{dB})$$

It is evident that for **this** example, the common-mode gain A_{cm} is **minimized**, and thus the CMRR is **maximized**, when:

$$R_1 R_4 = R_2 R_3$$

so that $R_1 R_4 - R_2 R_3 = 0$.