

2.4 Difference Amplifiers

Reading Assignment:

Op-amp circuits often have more than one inputs; the best way to analyze these circuits is with **superposition!**

HO: SUPERPOSITION AND OP-AMP CIRCUITS

Many two input op-amp circuits are differential amplifiers. These circuits should exhibit a large **common-mode rejection ratio!**

HO: DIFFERENTIAL AND COMMON MODE GAIN