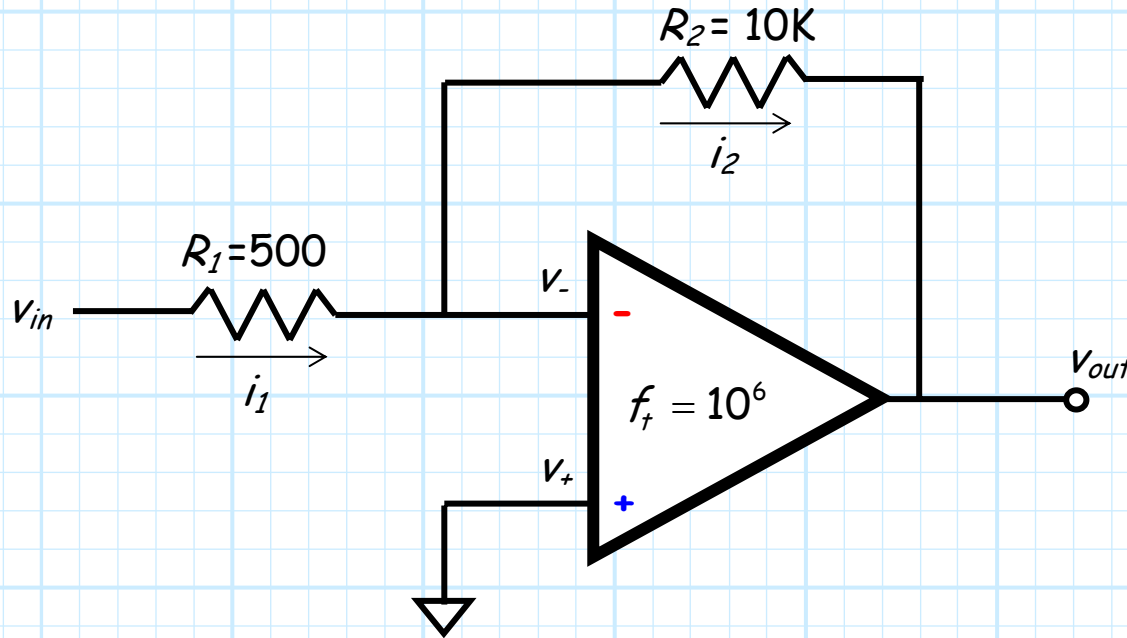


# Example: Amplifier Bandwidth

Say we build the following amplifier in the lab:



The op-amp in this circuit happens to have a unity-gain bandwidth of **1MHz**.

**Q:** *What is the 3 dB bandwidth of this amplifier?*

## $xy=10^6$ and $x=20$ ; you figure it out

**A:** We know that the mid-band **gain** of this amplifier is:

$$|A_{vo}(\omega_m)| = \left| \frac{-R_2}{R_1} \right| = \frac{R_2}{R_1} = \frac{10}{0.5} = 20 \quad (26\text{dB})$$


Since we know that  $f_T = 10^6$ , we can directly determine the amplifier **bandwidth**:

$$f_{3dB} = \frac{f_T}{|A_{vo}(f_m)|} = \frac{10^6}{20} = 5 \times 10^4$$

Since the **product** of the amplifier **gain** and **bandwidth** is equal to the **gain-bandwidth product**, we find that the gain-bandwidth product  $f_T$  **divided** by the mid-band **gain** equals the amplifier **bandwidth**  $f_{3dB}$ !
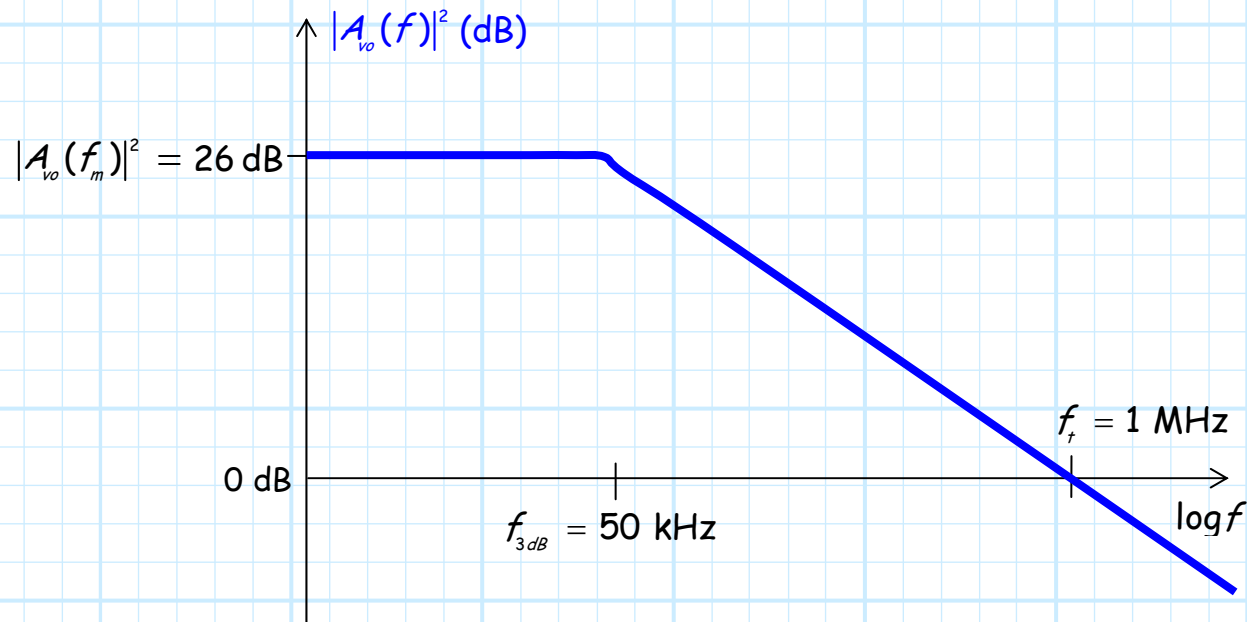
## If I want more bandwidth...

In this case, the amplifier bandwidth is  $f_{3dB} = 50 \text{ kHz}$ .



**Q:** *Is there any way to **increase** the bandwidth of this amplifier to  $500 \text{ kHz}$ ?*

**A:** Sure! But we must **decrease** its mid-band gain.

## ...I must accept less gain

The gain-bandwidth product  $f_t = 10^6$  is a constant—if we **increase** the bandwidth, we must **decrease** the gain.

Therefore, if we want the amplifier bandwidth to equal 500 kHz, we must **decrease** the mid-band gain to:

$$|A_{vo}(f_m)| = \frac{f_t}{f_{3dB}} = \frac{10^6}{5 \times 10^5} = 2 \quad (6\text{dB})$$

A gain of 2—**quite** a decrease!

But this of course **makes sense**.

To **increase** the bandwidth **10 times**, we must **decrease** the gain by a factor of **10**.

# There's no free lunch

Note we **could** accomplish this by simply changing the **feedback resistor** from  $R_2 = 10K$  to  $R_2 = 1K$ .

