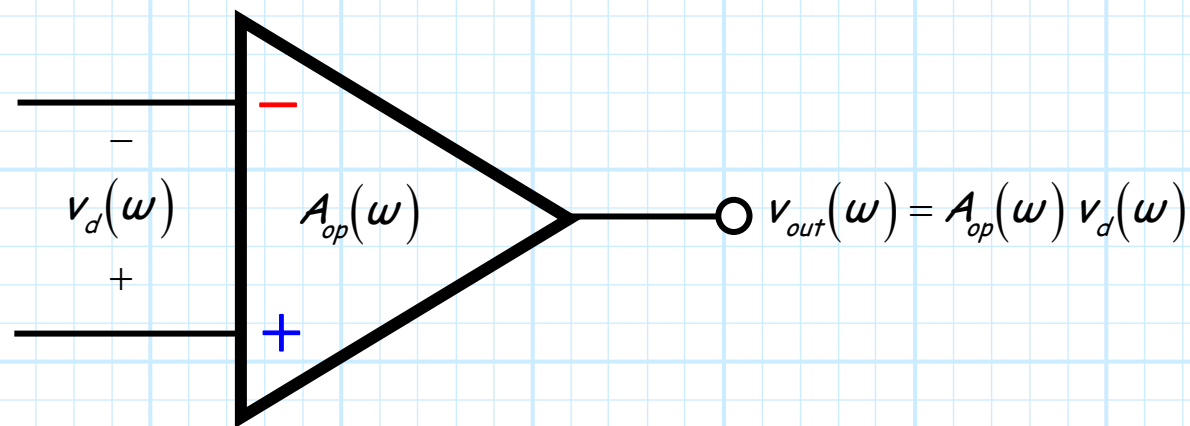


The Gain of Real Op-Amps

The **open-circuit** voltage gain A_{op} (a **differential** gain!) of a **real** (i.e., **non-ideal**) operational amplifier is **very large** at D.C. (i.e., $\omega = 0$), but gets **smaller** as the signal frequency ω **increases**!

In other words, the **differential** gain of an op-amp (i.e., the **open-loop** gain of a feedback amplifier) is a function of frequency ω .

We will thus express this gain as a **complex** function in the **frequency domain** (i.e., $A_{op}(\omega)$).



Gain is a complex function frequency

Typically, this op-amp behavior can be described mathematically with the **complex** function:

$$A_{op}(\omega) = \frac{A_0}{1 + j\left(\frac{\omega}{\omega_b}\right)}$$

or, using the frequency definition $\omega = 2\pi f$, we can write:

$$A_{op}(f) = \frac{A_0}{1 + j\left(\frac{f}{f_b}\right)}$$

where ω is frequency expressed in units of **radians/sec**, and f is signal frequency expressed in units of **cycles/sec**.

DC is when the signal frequency is zero

Note the squared **magnitude** of the op-amp gain is therefore the **real** function:

$$\begin{aligned} |A_{op}(\omega)|^2 &= \frac{A_0}{1 + j(\omega/\omega_b)} \frac{A_0}{1 - j(\omega/\omega_b)} \\ &= \frac{A_0^2}{1 + (\omega/\omega_b)^2} \end{aligned}$$

Therefore at **D.C.** ($\omega = 0$) the op-amp gain is:

$$A_{op}(\omega = 0) = \frac{A_0}{1 + j(0/\omega_b)} = A_0$$

and thus:

$$|A_{op}(\omega = 0)|^2 = A_0^2$$

Where:

$$A_0 = \text{op-amp D.C. gain}$$

The break frequency

Again, note that the D.C. gain A_0 is:

- 1) an **open-circuit** voltage gain
- 2) a **differential** gain
- 3) also referred to as the **open-loop** D.C. gain

The open-loop gain of real op-amps is **very large**, but fathomable — typically between 10^5 and 10^8 .

Q: *So just what **does** the value ω_b indicate ?*

A: The value ω_b is the op-amp's **break frequency**.

Typically, this value is very **small** (e.g. $f_b = 10\text{Hz}$).

The 3dB bandwidth

To see **why** this value is **important**, consider the op-amp gain at $\omega = \omega_b$:

$$A_{op}(\omega = \omega_b) = \frac{A_0}{1 + j(\omega/\omega_b)} = \frac{A_0}{1 + j} = \frac{A_0}{2} - j\frac{A_0}{2} = \frac{|A_0|}{\sqrt{2}} e^{-j\pi/4}$$


The **squared magnitude** of this gain is therefore:

$$|A_{op}(\omega = \omega_b)|^2 = \frac{A_0}{1 + j} \frac{A_0}{1 - j} = \frac{A_0^2}{1 - j^2} = \frac{A_0^2}{2}$$

As a result, the **break** frequency ω_b is also referred to as the **"half-power"** frequency, or the **"3 dB"** frequency.

This value is very important!

If we plot $|A_{op}(\omega)|^2$ on a "log-log" scale, we get something like this:

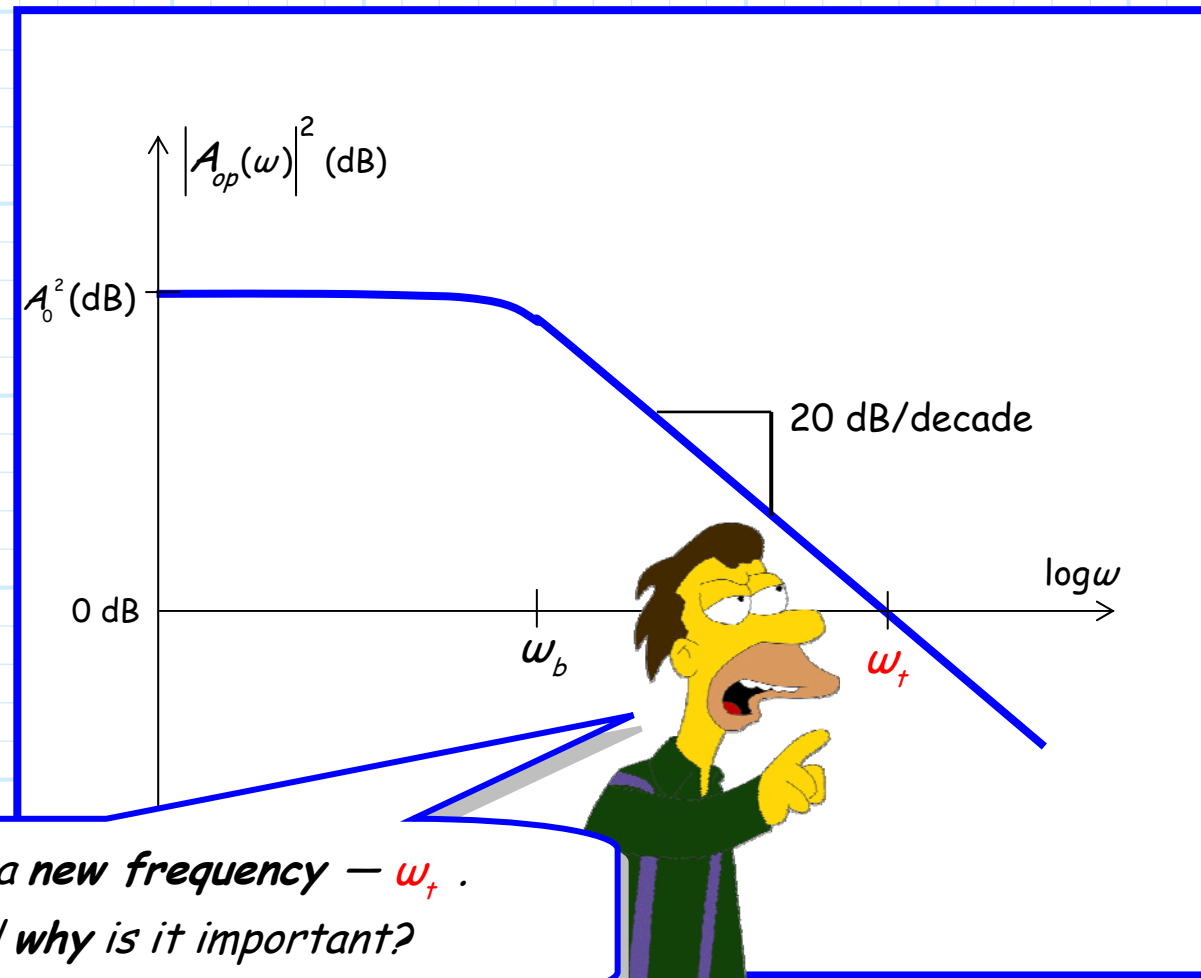

Q: Hey! You have defined a new frequency — ω_t .
What is this frequency and why is it important?

The unity gain frequency

A: Note that ω_t is the frequency where the magnitude of the gain is "unity" (i.e., where the gain is 1). I.E.,

$$|A_{op}(\omega = \omega_t)|^2 = 1$$

Note that when expressed in dB, **unity** gain is:

$$10 \log_{10} |A_{op}(\omega = \omega_t)|^2 = 10 \log_{10} (1) = 0 \text{ dB}$$

Therefore, on a "log-log" plot, the gain curve crosses the **horizontal axis** at frequency ω_t .

We thus refer to the frequency ω_t as the "**unity-gain frequency**" of the operational amplifier.

It's the product of the gain and the bandwidth!

Note that we can **solve** for this frequency in terms of **break frequency** ω_b and **D.C. gain** A_0 :

$$1 = \left| A_{op}(\omega = \omega_t) \right|^2 = \frac{A_0^2}{1 + \left(\frac{\omega_t}{\omega_b} \right)^2}$$

meaning that:

$$\omega_t^2 = \omega_b^2 (A_0^2 - 1)$$

But recall that $A_0 \gg 1$, therefore $A_0^2 - 1 \approx A_0^2$ and:

$$\omega_t = \omega_b |A_0|$$

Note since the frequency ω_b defines the 3 dB **bandwidth** of the op-amp, the unity gain frequency ω_t is simply the **product** of the op-amp's D.C. **gain** $|A_0|$ and its **bandwidth** ω_b .

It's not rocket science!

As a result, ω_f is alternatively referred to as the **gain-bandwidth product!**

$\omega_f \doteq$ **Unity Gain Frequency**

and

$\omega_f \doteq$ **Gain - Bandwidth Product**



*This is so **simple** perhaps even I can remember it:*

*The **gain-bandwidth-product** is the product of the gain and the bandwidth!*