

### Special Problem 2.6-1


The **input** to the circuit below is:

$$v_{in}(t) = 0.5 t^2 - 0.5 \text{ V}$$

where time  $t$  is in **microseconds**.

The **slew rate** of the op-amp is  $10 \text{ V}/\mu\text{sec}$ .

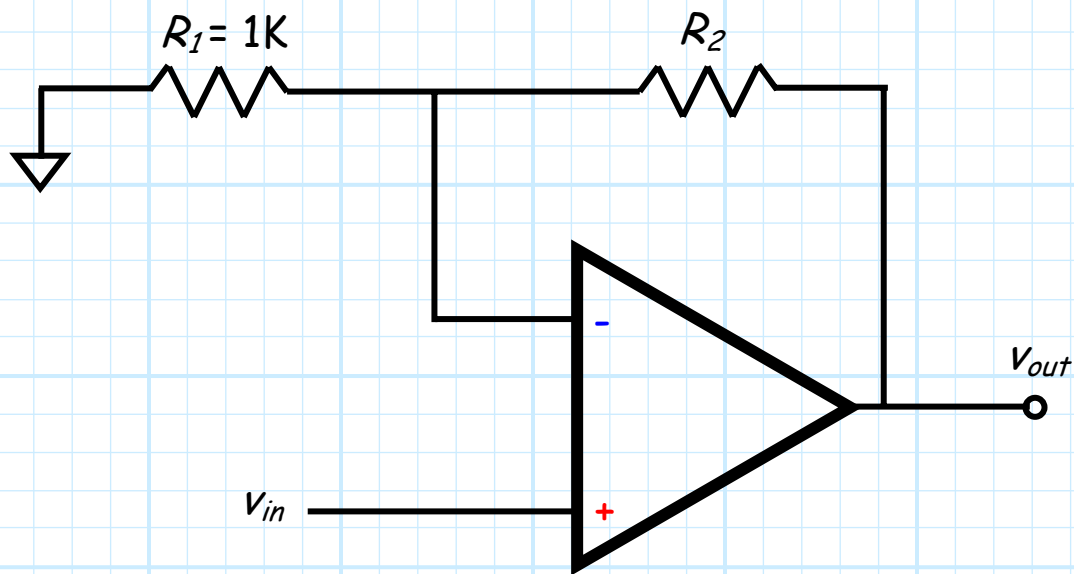The **DC power supplies** are  $V = 15 \text{ V}$  and  $V = -15 \text{ V}$ .



- 1) If  $R_2 = 1 \text{ K}$ , at what time  $t$  will the output signal  $v_{out}(t)$  begin to distort?
- 2) If  $R_2 = 9 \text{ K}$ , at what time  $t$  will the output signal  $v_{out}(t)$  begin to distort?