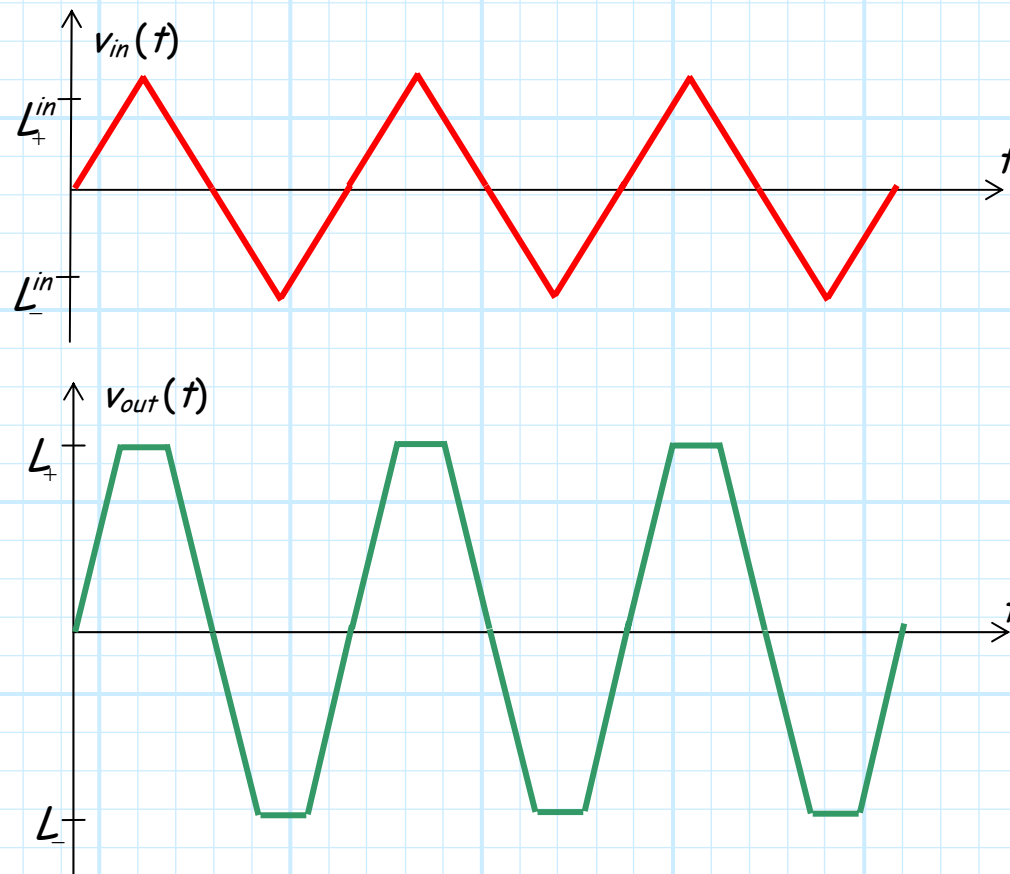


Slew Rate

We know that the output voltage of an amplifier circuit is **limited**, i.e.:

$$L_- < v_{out}(t) < L_+$$

During any period of time when the output tries to exceed these limits, the output will **saturate**, and the signal will be **distorted**! E.G.:



Limits on the time derivative

But, this is **not** the only way in which the output signal is **limited**, nor is saturation the only way it can be **distorted**!

A **very** important op-amp parameter is the **slew rate** (S.R.).

Whereas L_- and L_+ set limits on the values of output signal $v_{out}(t)$, the slew rate sets a limit on its **time derivative** !!!! I.E.:

$$-S.R. < \frac{d v_{out}(t)}{dt} < +S.R.$$

In other words, the output signal can **only change so fast**! Any attempt to exceed this fundamental op-amp limit will result in **slew-rate limiting**.

The red means distortion

So, in addition to **saturation**:

$$v_{out}(t) = \begin{cases} L_+ & \text{if } A_{vo} v_{in}(t) > L_+ \\ A_{vo} v_{in}(t) & \text{if } L_- < A_{vo} v_{in}(t) < L_+ \\ L_- & \text{if } L_- > A_{vo} v_{in}(t) \end{cases}$$

we find the following **output** signal condition:


$$v_{out}(t) = \begin{cases} A_{vo} v_{in}(t) & \text{if } \left| \frac{d A_{vo} v_{in}(t)}{dt} \right| < S.R. \\ \pm(S.R.)t + C & \text{if } \left| \frac{d A_{vo} v_{in}(t)}{dt} \right| > S.R. \end{cases}$$

For example

For example, say we build a **non-inverting** amplifier with mid-band gain $A_{vo} = 2$.

This amplifier was constructed using an op-amp with a **slew rate** equal to $4\text{V}/\mu\text{sec}$.

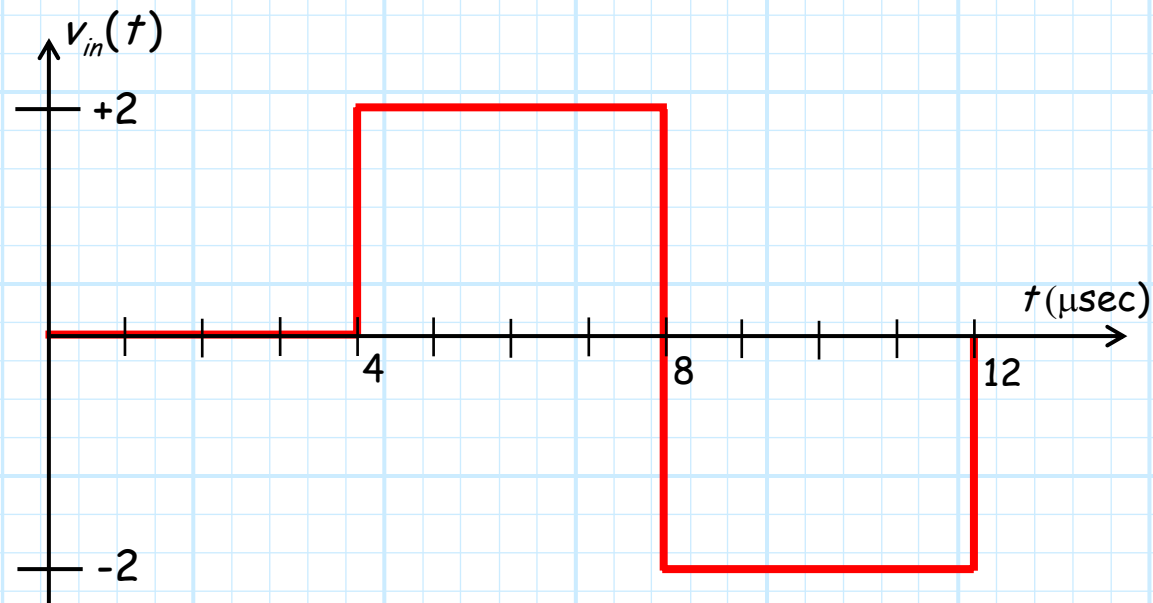
Q: *If we input the following signal $v_{in}(t)$, what will we see at the **output** of this amplifier?*



This is what it should look like

A: Ideally, the output would look exactly like the input, only multiplied by $A_{vo} = 2$:
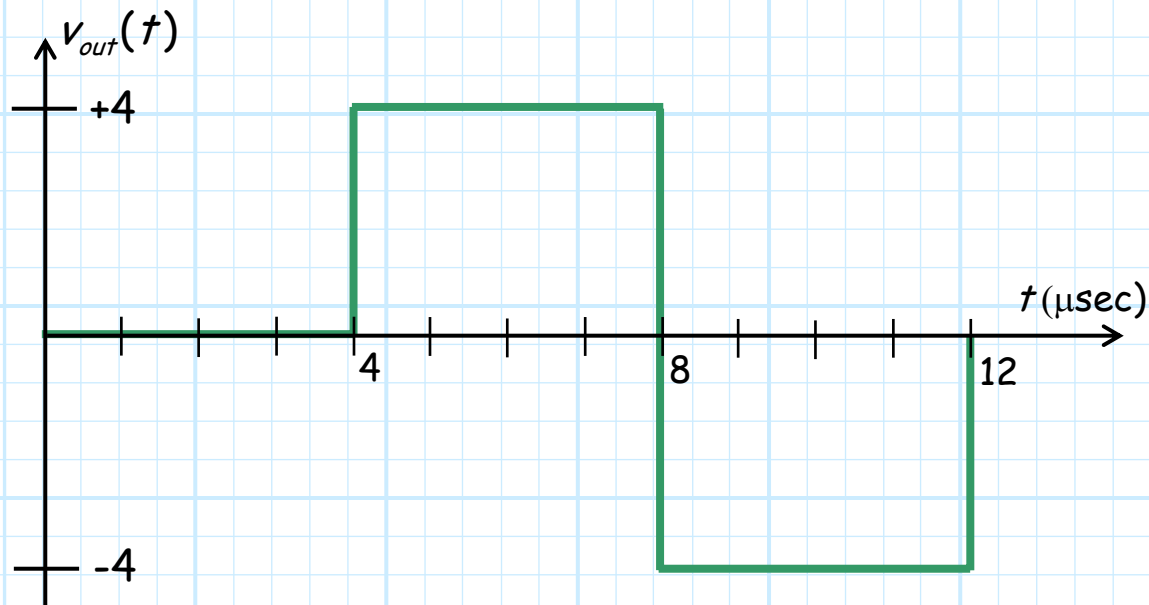
$$v_{out}(t) = 2 v_{in}(t) \quad (\text{ideal})$$



Note that the time derivative of this output is **zero** at **almost** every time t :

$$\frac{dv_{out}(t)}{dt} = 0 \quad \text{for almost all time } t$$

Now you see the problem!

The **exceptions** are at times $t=4$, $t=8$, and $t=12$ μsec , where we find that the time derivative is **infinite!**


$$\frac{dv_{out}(t)}{dt} = \infty \quad \text{at times } t = 4 \text{ and } t = 12$$

and

$$\frac{dv_{out}(t)}{dt} = -\infty \quad \text{at time } t = 8$$

This is a **problem!**


$$\left| \frac{dv_{out}(t)}{dt} \right| = \infty > 4V/\mu\text{sec} \text{ !!!!}$$

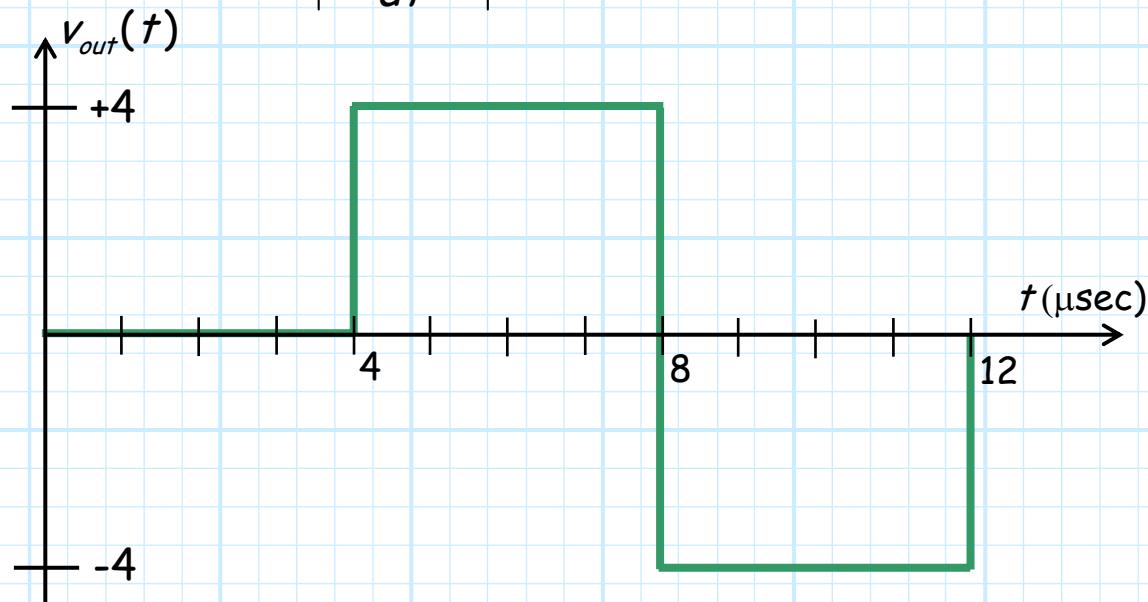

This is what it actually looks like!

Thus, the output signal **exceeds** the slew rate of the op-amp—or at least, it **tries** too!

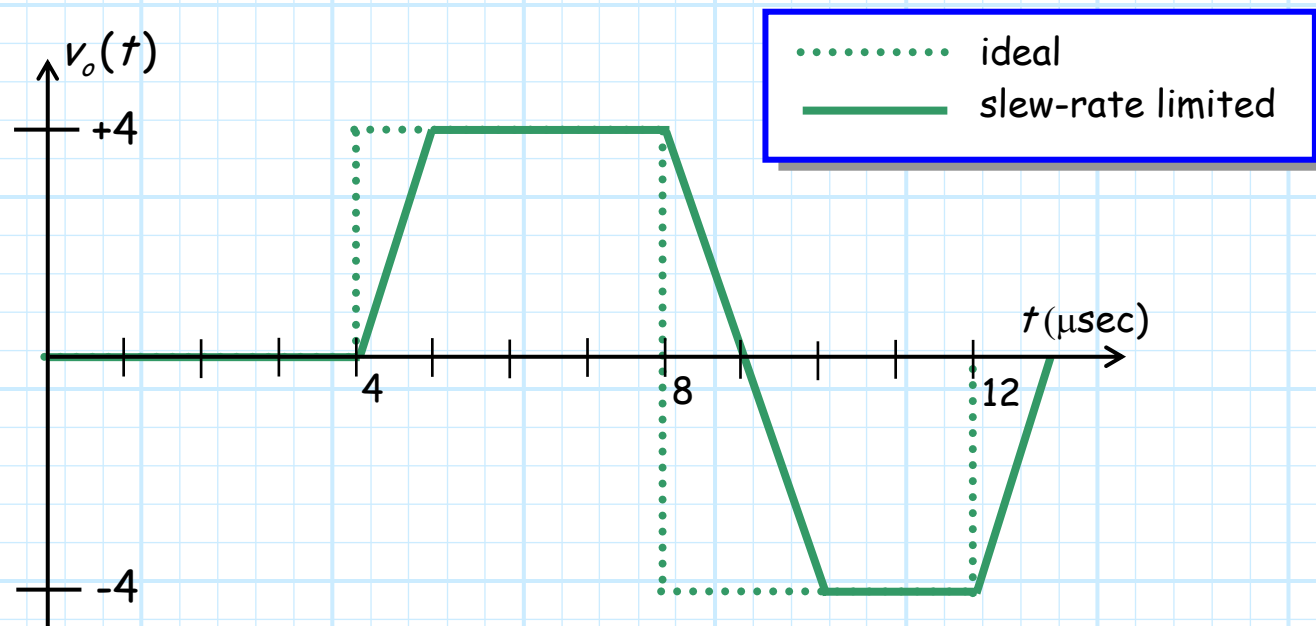The reality is that since the op-amp output **cannot** change at a rate greater than $\pm 4\text{V}/\mu\text{sec}$, the output signal will be **distorted!**



Note the derivative of the **actual** output signal is limited to a maximum value ($\pm 4\text{V}/\mu\text{sec}$) by the op-amp **slew rate**.