
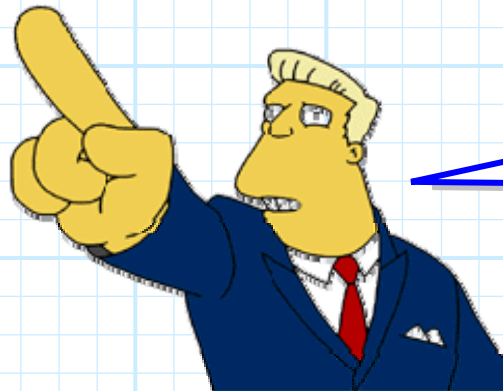

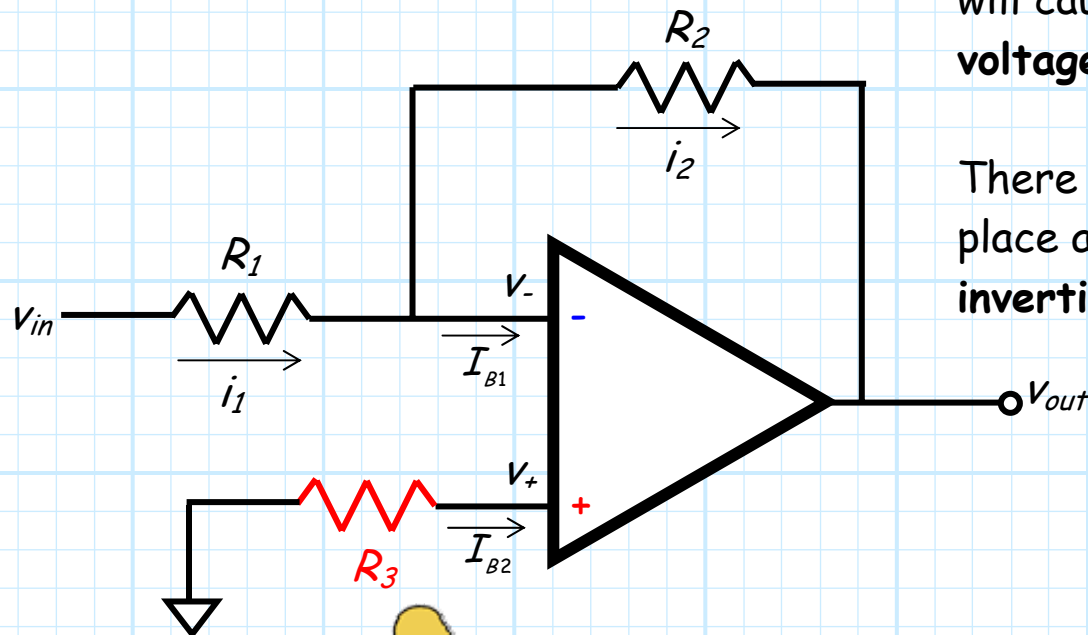
# Reducing the Effect of Input Bias Current

We found that the input bias current will cause an **offset** in the **output voltage**.

There is a **solution** to this problem—place a **resistor** ( $R_3$ ) on the **non-inverting input**!



**Q:** *Maria, why is this resistor here? I don't see how it can do any good.*

## The voltage $v_+$ is non-zero!

**A:** Let's **analyze** this circuit to determine how this new resistor helps.

First, notice that the voltage at the **non-inverting** terminal is now **non-zero!**

The bias current  $I_{B2}$  means that, by virtue of KVL:

$$v_+ = 0 - R_3 I_{B2} = -R_3 I_{B2}$$

Now, because of the **virtual short**:


$$v_- = v_+ = -R_3 I_{B2}$$

And from KCL:

$$i_1 = i_2 + I_{B1}$$

where from KCL and Ohm's Law:
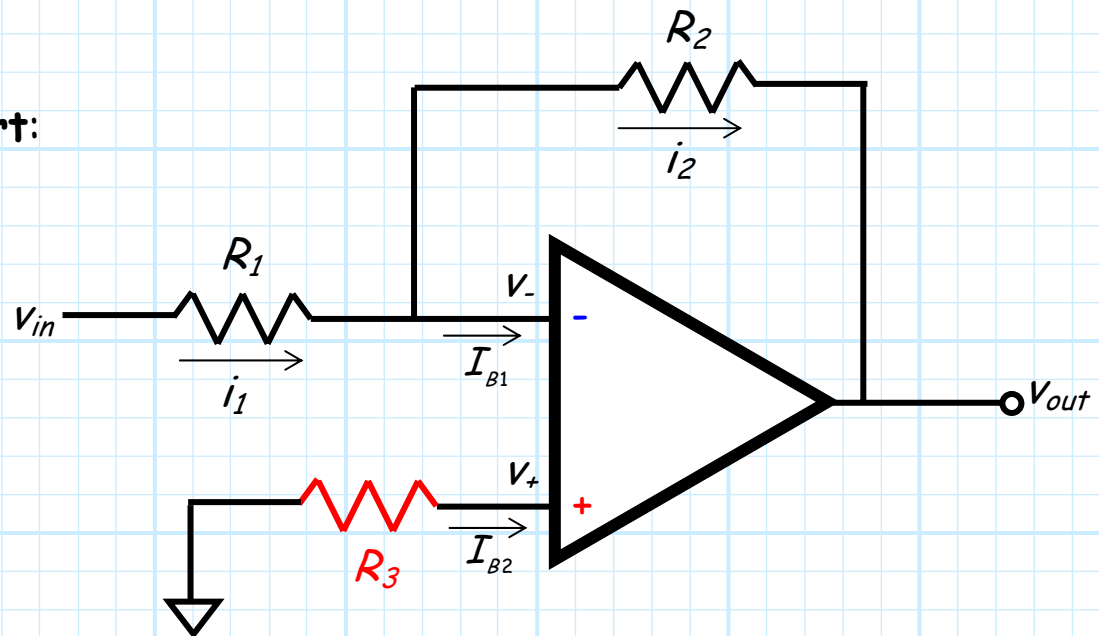
$$i_1 = \frac{v_{in} - v_-}{R_1} = \frac{v_{in} + R_3 I_{B2}}{R_1}$$




## It seems like this just made the offset even larger

And also from KCL and Ohm's Law:

$$i_2 = \frac{v_{in} - v_{out}}{R_2} = \frac{-(R_3 I_{B2} + v_{out})}{R_2}$$

Combining these results:
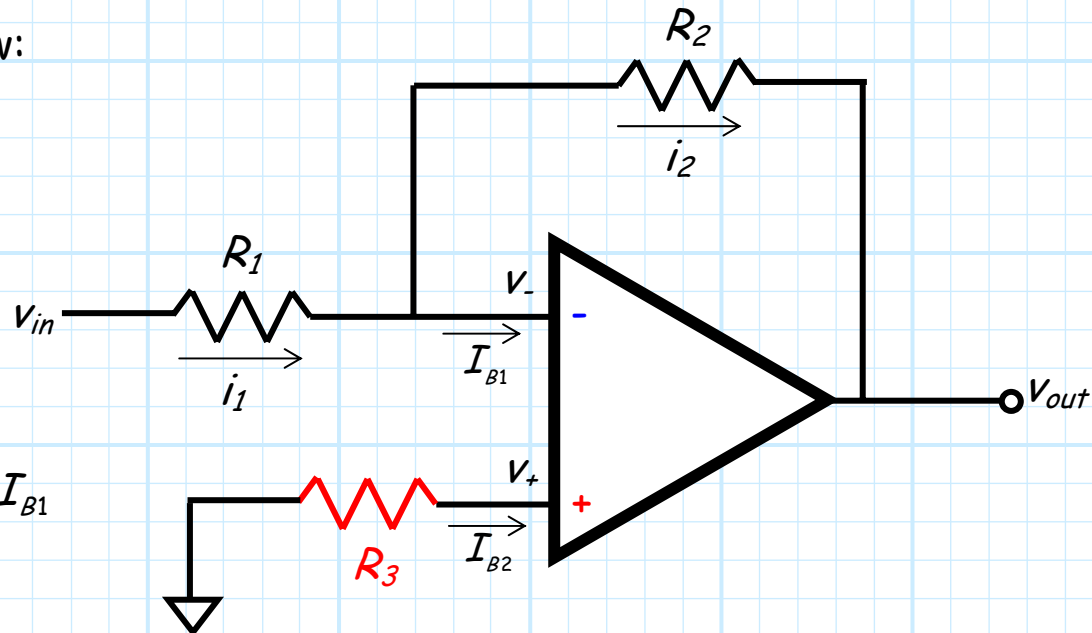
$$\frac{v_{in} + R_3 I_{B2}}{R_1} = \frac{-(R_3 I_{B2} + v_{out})}{R_2} + I_{B1}$$



Performing the usual algebraic gymnastics, we **rearrange** this result and find that the **output voltage** is:


$$v_{out} = \left( -\frac{R_2}{R_1} \right) v_{in} - \left( R_3 I_{B2} + \frac{R_2 R_3}{R_1} I_{B2} - R_2 I_{B1} \right)$$

## Awl be baak

Again we find the output consists of **two** terms. The first term is the **ideal** inverting amplifier result:

$$-\frac{R_2}{R_1} v_{in}$$

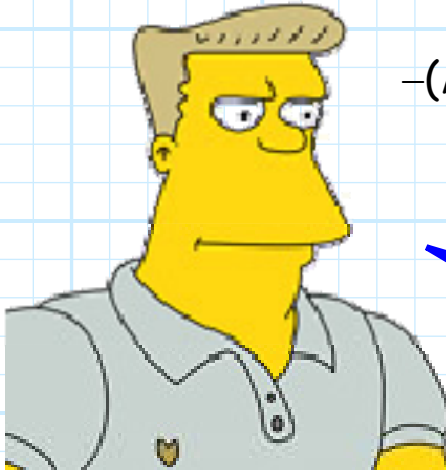and the second is an output **D.C. offset**:



$$-(R_3 I_{B2} + \frac{R_2 R_3}{R_1} I_{B2} - R_2 I_{B1})$$

**Q:** Resistor  $R_3$  was supposed to **reduce** the D.C. offset, but it seems to have made things even **worse**. Fix this or I shall be forced to pummel you.

## We must choose the proper value of $R_3$ ...

**A:** Say we set the value of resistor  $R_3$  to equal  $R_3 = R_1 \parallel R_2$ , i.e.:

$$R_3 = \frac{R_1 R_2}{R_1 + R_2}$$

In this case, the **D.C. offset** becomes:

$$\begin{aligned} & - \left( \frac{R_1 R_2}{R_1 + R_2} I_{B2} + \frac{R_2^2}{R_1 + R_2} I_{B2} - R_2 I_{B1} \right) \\ & = - \left( \frac{(R_1 + R_2) R_2}{R_1 + R_2} I_{B2} - R_2 I_{B1} \right) \\ & = R_2 (I_{B1} - I_{B2}) \\ & = R_2 I_{os} \end{aligned}$$

Typically, the bias currents  $I_{B1}$  and  $I_{B2}$  are approximately equal, so that **offset current**  $I_{B1} - I_{B2} = I_{os}$  is very **tiny**.

Therefore, the resulting output **offset voltage** is likewise very **tiny!**




## ...and this is that proper value

Therefore, when designing an amplifier with **real** op-amps, **always** include a resistor  $R_3$  equal to the value:

$$R_3 = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

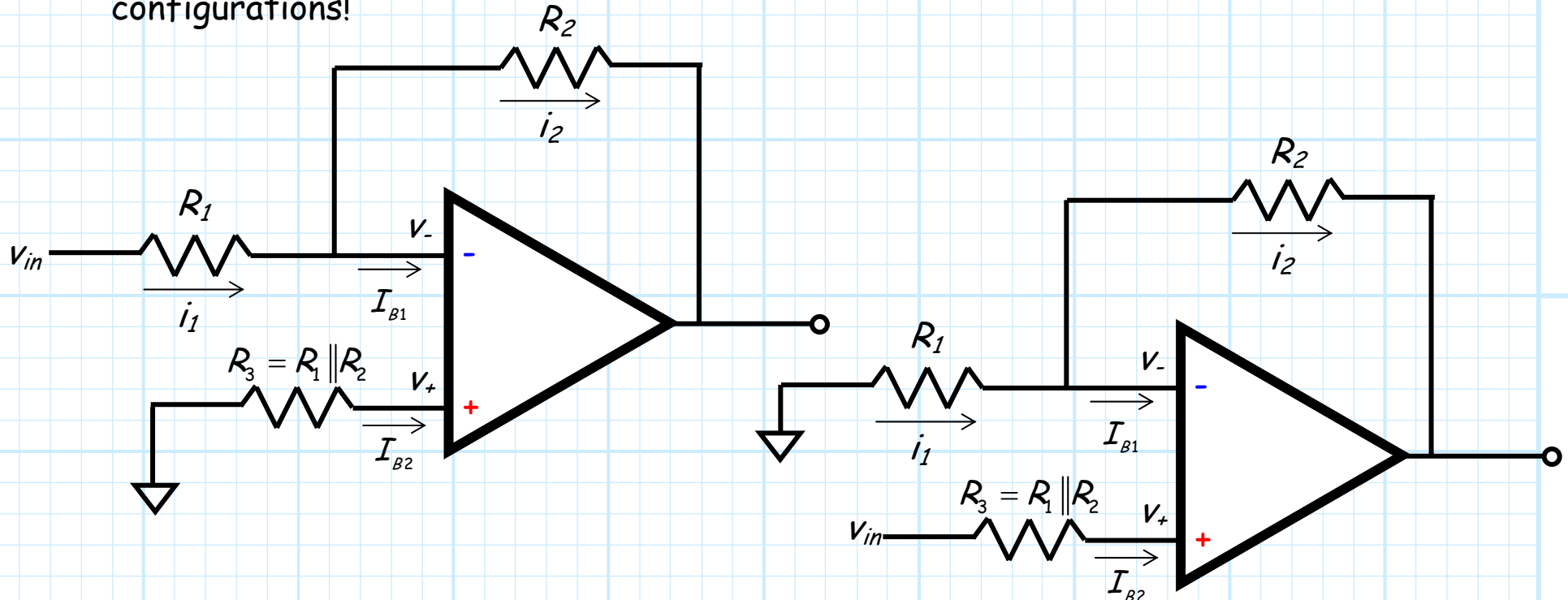This is true **regardless** of whether we use the **inverting** or **non-inverting** configurations!



## This is just the type of subtle point that shows up on an exam

If the impedances are **complex** (i.e.,  $Z_1(\omega)$  and  $Z_2(\omega)$ ), then set the resistor  $R_3$  based on the D.C. values of the impedances:

$$R_3 = Z_1(\omega = 0) \parallel Z_2(\omega = 0)$$

In other words, set the **capacitors** to **open** circuits and **inductors** to **short** circuits.