

Special Problem 2.6-5


The op-amp in the circuit below has a **slew rate** of 10 volts/ μ sec.

Its **output** voltage is **limited** to $-15 < v_{out}(t) < 15$ (otherwise the output **saturates**).

The **input** signal is:

$$v_{in}(t) = 0.25t^2 \text{ V}$$

where time t is in **microseconds**.

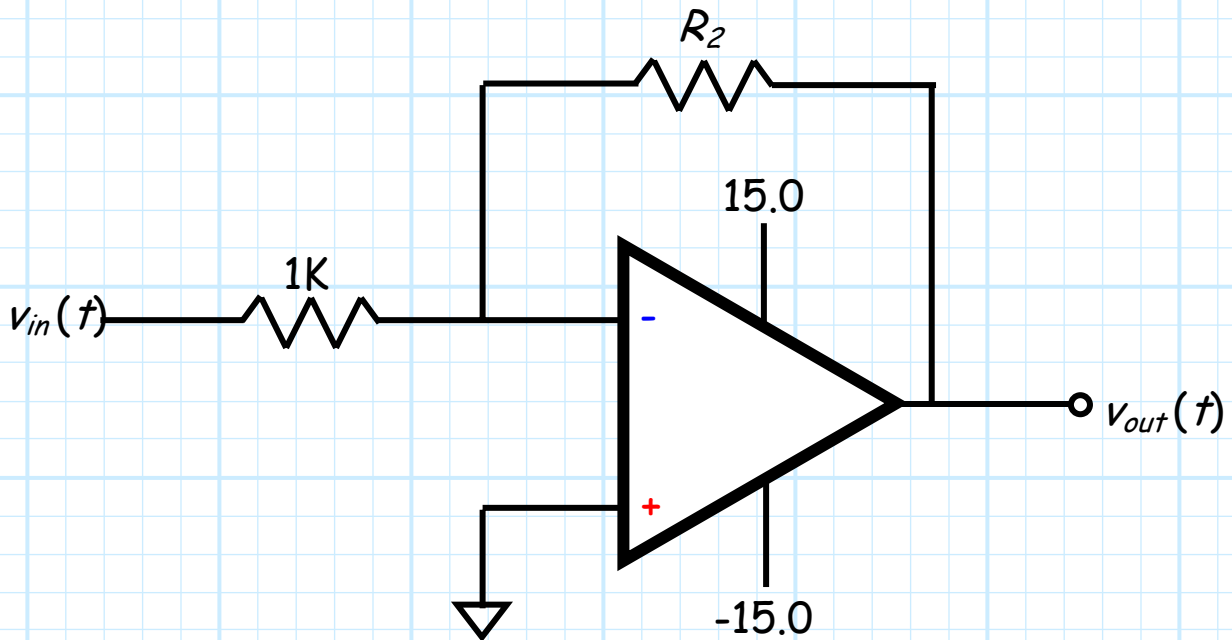

Determine the **time** t (in microseconds) when the output signal $v_{out}(t)$ begins to **distort** for **any reason**, if:

- a) $R_2 = 3K$
- b) $R_2 = 15K$