

Special Problem 2.7-1

Determine the value of resistor R_3 that will minimize the output offset voltage of this amplifier, due to input bias current.

Hint: Do not spend too much time on this problem!

