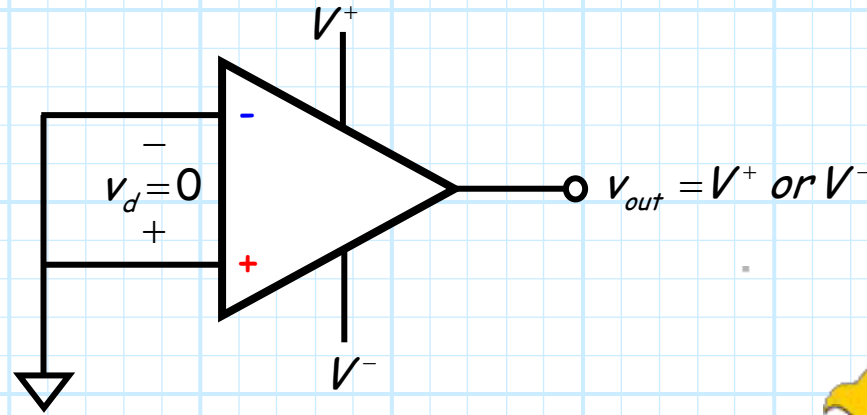


# The Input Offset Voltage

For real op-amps, we typically find that if both inputs are grounded, the output will be—**saturated**!



**Q:** *What!? Why isn't*

$$\begin{aligned} v_{out}(t) &= A_{op} v_d \\ &= A_{op}(0) ?? \\ &= 0 \end{aligned}$$




**A:** The reason the output is saturated is that real op-amps exhibit a phenomenon called the **input offset voltage**  $V_{os}$ .

# The input offset voltage model

This value can be either positive or negative, typically with a magnitude of 5 mV or less ( $|V_{os}| < 5 \text{ mV}$ ).

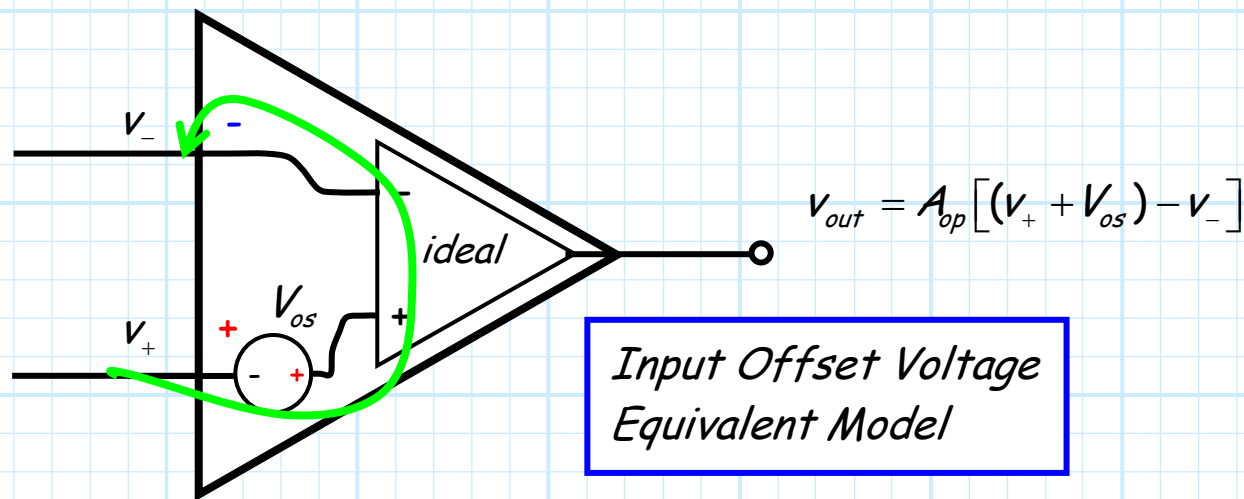A real op-amp therefore behaves as if it has a small, **internal voltage source** at the non-inverting input:



Applying the concept of a virtual short to the **ideal** op-amp, we find from **KVL**

$$v_- = v_+ + V_{os}$$

Thus,  $v_- \neq v_+$ !

## The new virtual "short"

Recall, however, that the input offset voltage is typically **very small** (i.e.,  $|V_{os}| < 5\text{ mV}$ ), so that  $v_- \approx v_+$ .


So, for an op-amp with an **input offset voltage**, the virtual "short" equation turns out to be:

$$v_- = V_{os} + v_+$$
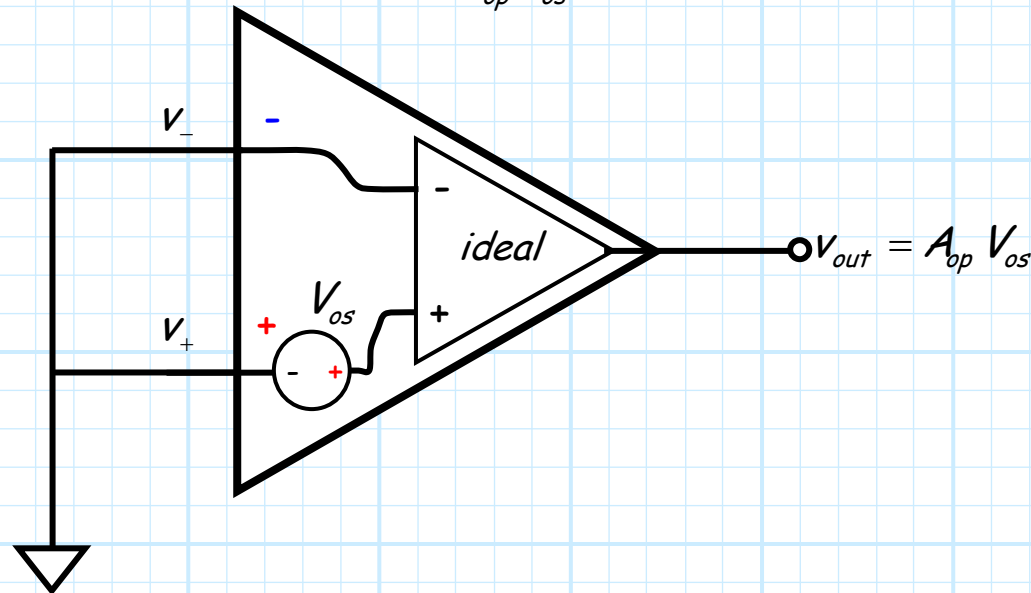
## Small, but large enough to saturate!

Therefore, if  $v_- = v_+ = 0$ , we find that the output voltage of this op-amp is **ideally** equal to:

$$\begin{aligned} v_{out} &= A_{op} (v_+ - v_- + V_{os}) \\ &= A_{op} (0 - 0 + V_{os}) \\ &= A_{op} V_{os} \end{aligned}$$



Of course, since the differential voltage  $A_{op}$  is **very** large, the product  $A_{op} V_{os}$  is likewise large, such that the output of **real** op-amps will **saturate**.

## This changes our previous results

**Q:** Does this mean that  $V_{os}$  will cause the output of op-amp circuits and amplifiers to saturate?

**A:** Fortunately no!

However, the input offset voltage **will** affect the **output** of circuits and amplifiers made with op-amps.

