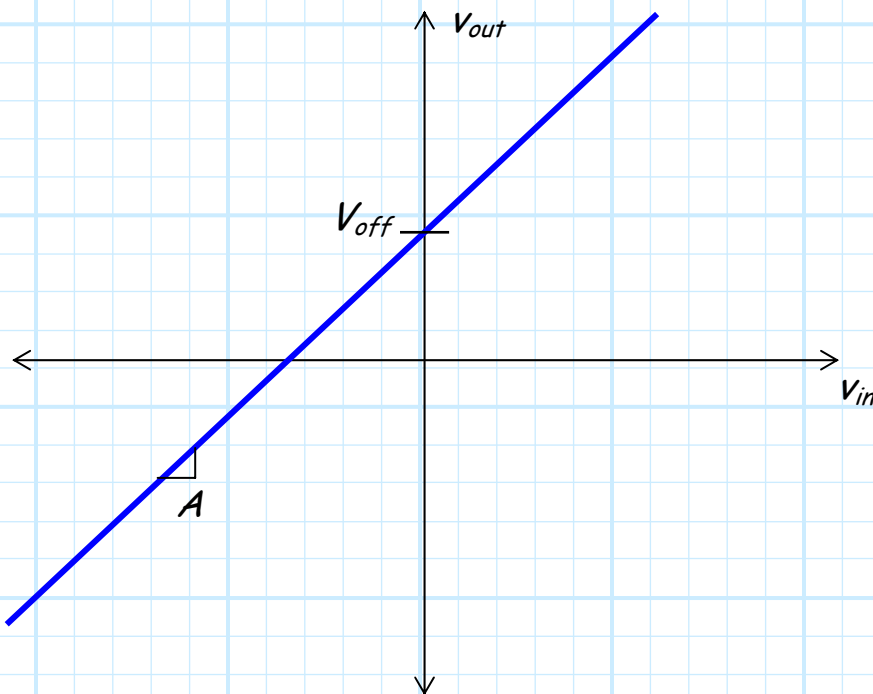


## 2.7 DC Imperfections

**Reading Assignment: 98-104**

In **addition** to saturation and slew-rate limiting, **another** non-linear behavior of amplifiers is a **DC output offset!**



Amplifiers built with op-amps can/will exhibit this non-linear behavior, mainly for **two** separate reasons!

**HO: THE INPUT OFFSET VOLTAGE**

**EXAMPLE: THE INPUT OFFSET VOLTAGE**

The **second** reason for output offsets is there is a constant **bias current** flowing into the input terminals.

### HO: THE INPUT BIAS CURRENT

### EXAMPLE: THE INPUT BIAS CURRENT

Fortunately, we can **minimize** the DC output offset due the input bias current with **one simple design rule**.


### HO: REDUCING THE EFFECT OF THE INPUT BIAS CURRENT

Finally, we find that real op-amps have **input** and **output** resistances that are not **quite** ideal!

### HO: REAL OP-AMP INPUT AND OUTPUT RESISTANCES
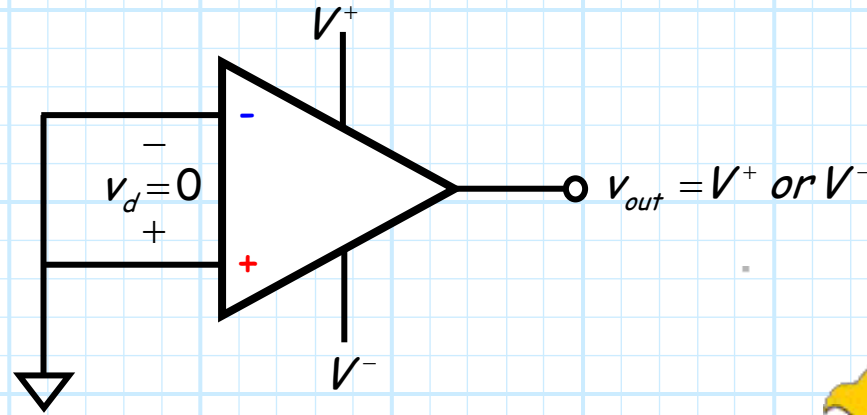
# The Input Offset Voltage

For real op-amps, we typically find that if both inputs are grounded, the output will be—**saturated**!



**Q:** *What!? Why isn't*

$$\begin{aligned} v_{out}(t) &= A_{op} v_d \\ &= A_{op}(0) ?? \\ &= 0 \end{aligned}$$




**A:** The reason the output is saturated is that real op-amps exhibit a phenomenon called the **input offset voltage**  $V_{os}$ .

# The input offset voltage model

This value can be either positive or negative, typically with a magnitude of 5 mV or less ( $|V_{os}| < 5 \text{ mV}$ ).

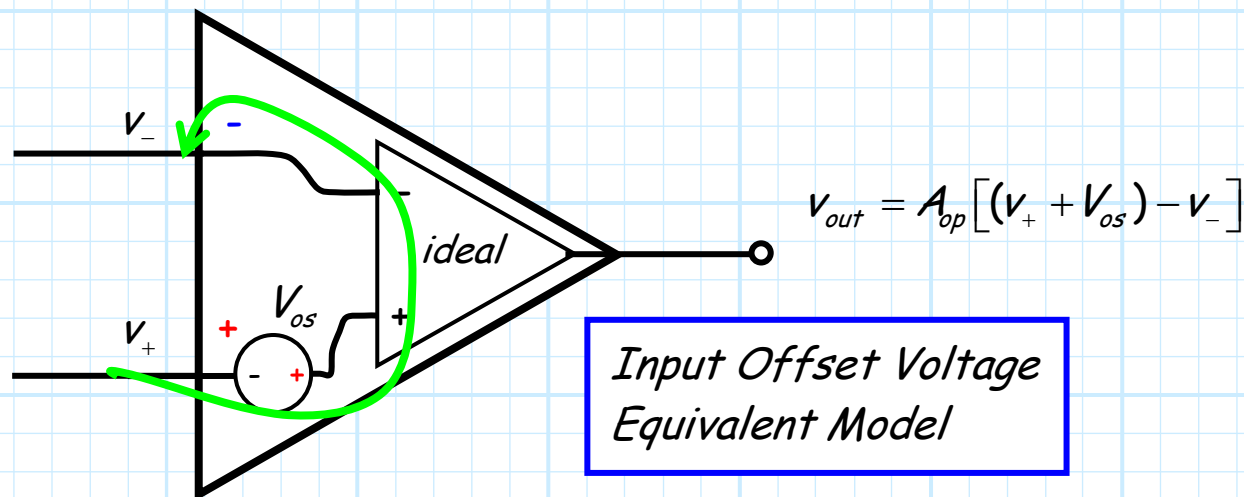A real op-amp therefore behaves as if it has a small, **internal voltage source** at the non-inverting input:



Applying the concept of a virtual short to the **ideal** op-amp, we find from **KVL**

$$v_- = v_+ + V_{os}$$

Thus,  $v_- \neq v_+$ !

## The new virtual "short"

Recall, however, that the input offset voltage is typically **very small** (i.e.,  $|V_{os}| < 5\text{ mV}$ ), so that  $v_- \approx v_+$ .


So, for an op-amp with an **input offset voltage**, the virtual "short" equation turns out to be:

$$v_- = V_{os} + v_+$$
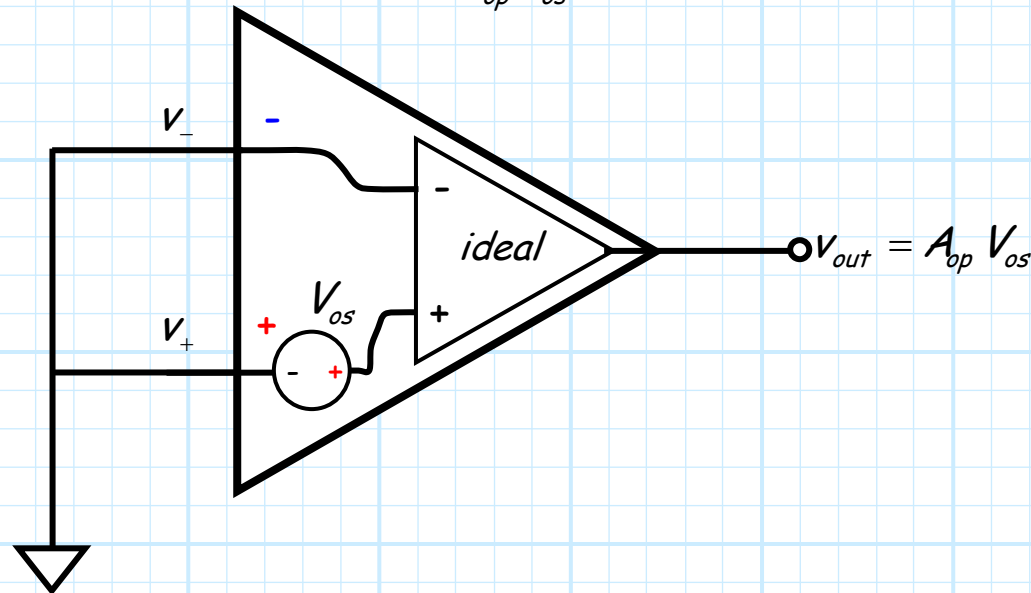
## Small, but large enough to saturate!

Therefore, if  $v_- = v_+ = 0$ , we find that the output voltage of this op-amp is **ideally** equal to:

$$\begin{aligned} v_{out} &= A_{op} (v_+ - v_- + V_{os}) \\ &= A_{op} (0 - 0 + V_{os}) \\ &= A_{op} V_{os} \end{aligned}$$




Of course, since the differential voltage  $A_{op}$  is **very** large, the product  $A_{op} V_{os}$  is likewise large, such that the output of **real** op-amps will **saturate**.

## This changes our previous results

**Q:** Does this mean that  $V_{os}$  will cause the output of op-amp circuits and amplifiers to saturate?


**A:** Fortunately no!

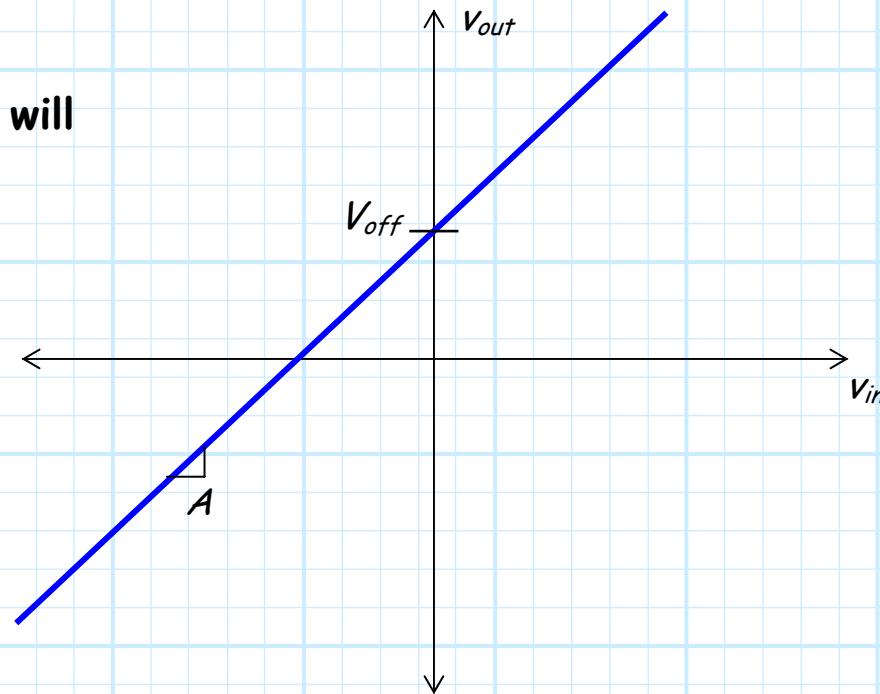However, the input offset voltage **will** affect the **output** of circuits and amplifiers made with op-amps.


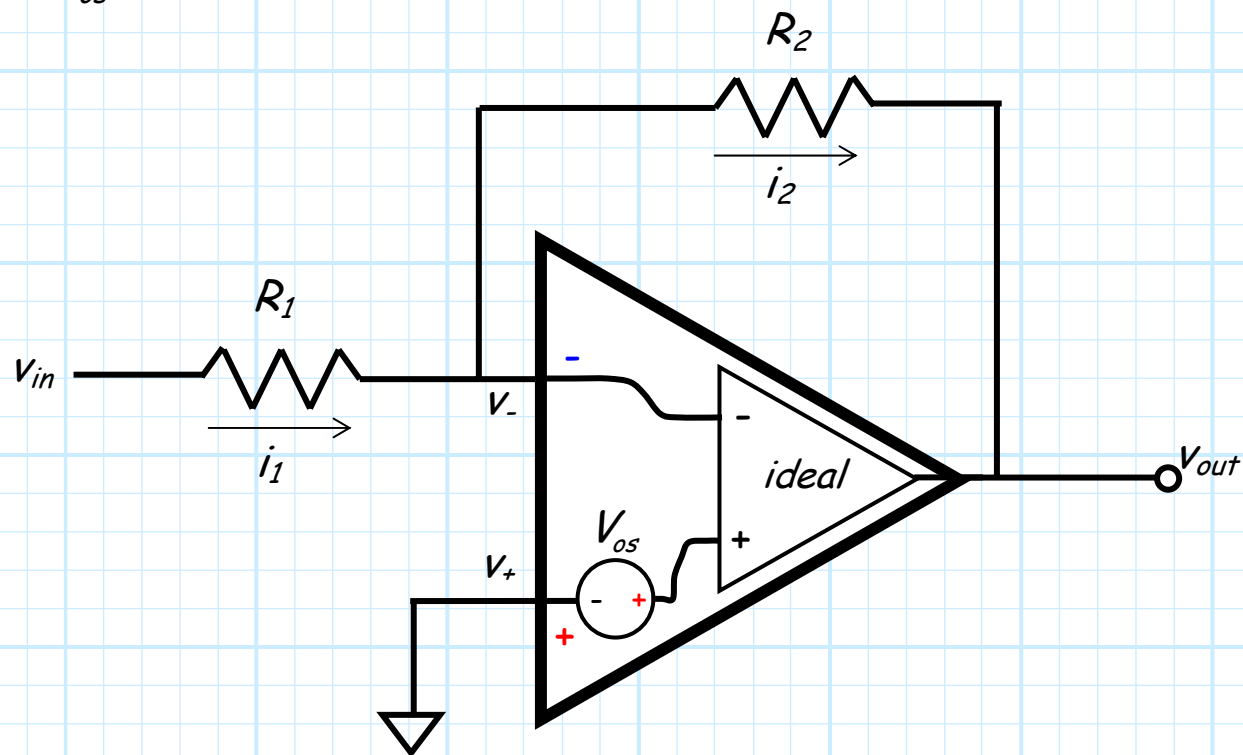
# Example: The Input Offset Voltage

Consider an **inverting** amp constructed with an op-amp exhibiting an **input offset voltage** of  $V_{os}$ :





## $v_-$ not equal to $v_+$

We know that because of the input offset voltage:

$$v_- = v_+ + V_{os}$$

For the circuit above, the non-inverting terminal of the op-amp is connected to ground (i.e.,  $v_+ = 0$ ), and so the virtual "ground" is now described by:

$$v_- = V_{os}$$

The **current** into each terminal of the op-amp is still **zero**, so that from KCL:

$$i_1 = i_2$$

where from KCL and Ohm's Law:

$$i_1 = \frac{v_{in} - v_-}{R_1} = \frac{v_{in} - V_{os}}{R_1}$$

and:

$$i_2 = \frac{v_- - v_{out}}{R_2} = \frac{V_{os} - v_{out}}{R_2}$$

# The output has a DC offset!

Combining, we find:


$$\frac{v_{in} - V_{os}}{R_1} = \frac{V_{os} - v_{out}}{R_2}$$

Performing a little algebra, we can solve this equation for **output voltage**  $v_{out}$ :

$$v_{out} = \frac{V_{os}R_1 + V_{os}R_2 - v_{in}R_2}{R_1}$$

and rearranging:

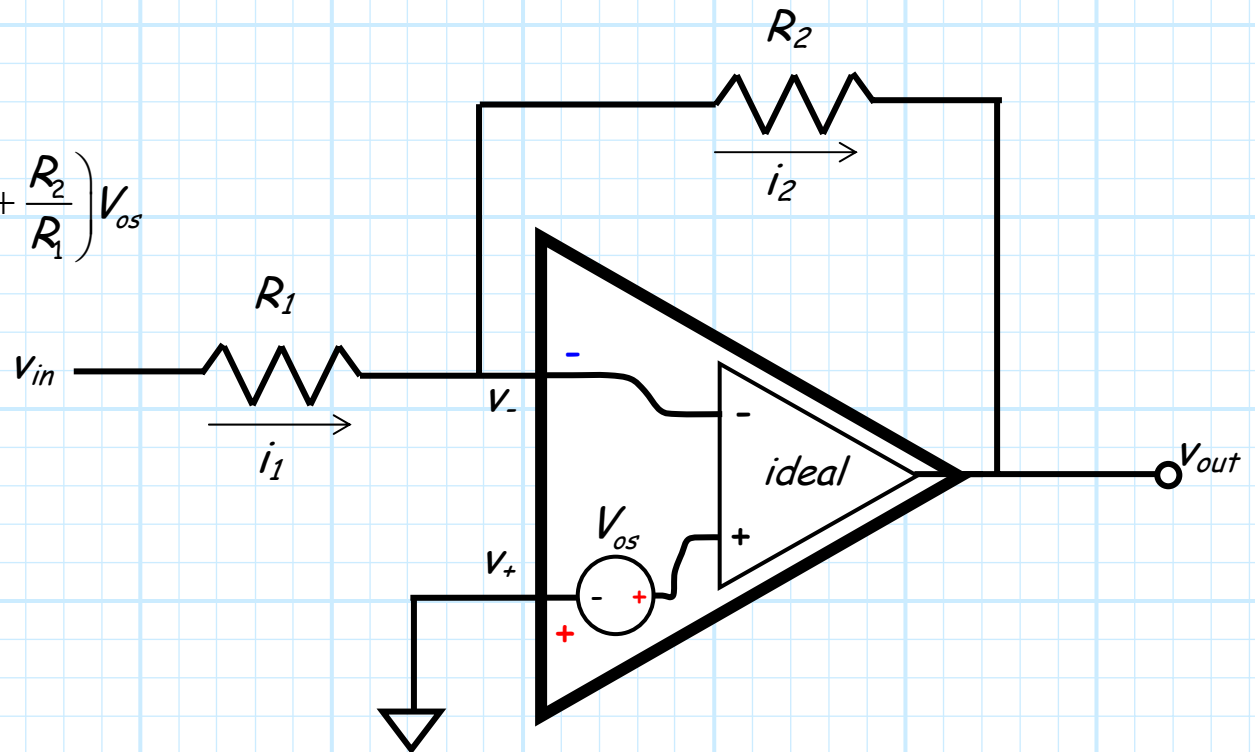
$$v_{out} = -\left(\frac{R_2}{R_1}\right)v_{in} + \left(1 + \frac{R_2}{R_1}\right)V_{os}$$



## Superposition is your friend

**Q:** Hey! Couldn't we have easily found this result by applying **superposition**?

**A:** Absolutely!

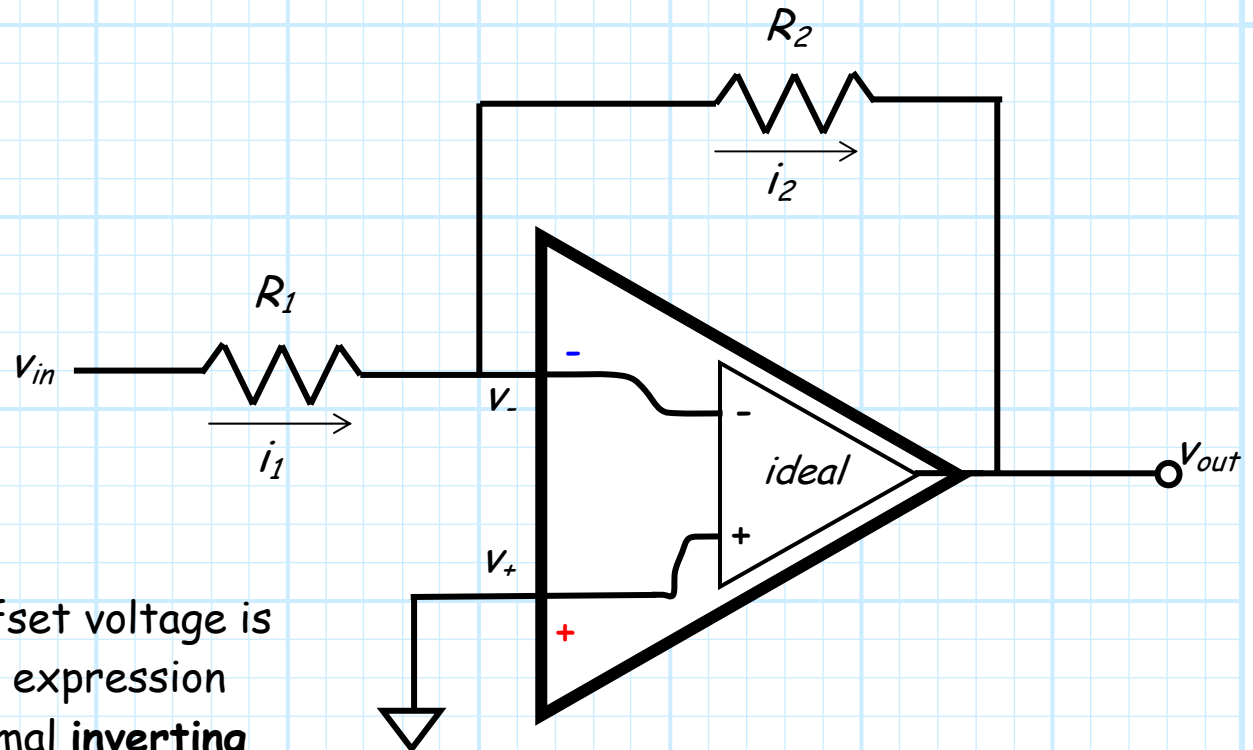


Note that if the input offset voltage is zero (its **ideal** value), this expression simply reduces to the normal **inverting amplifier** expression:

$$V_{out} = -\left(\frac{R_2}{R_1}\right)V_{in}$$
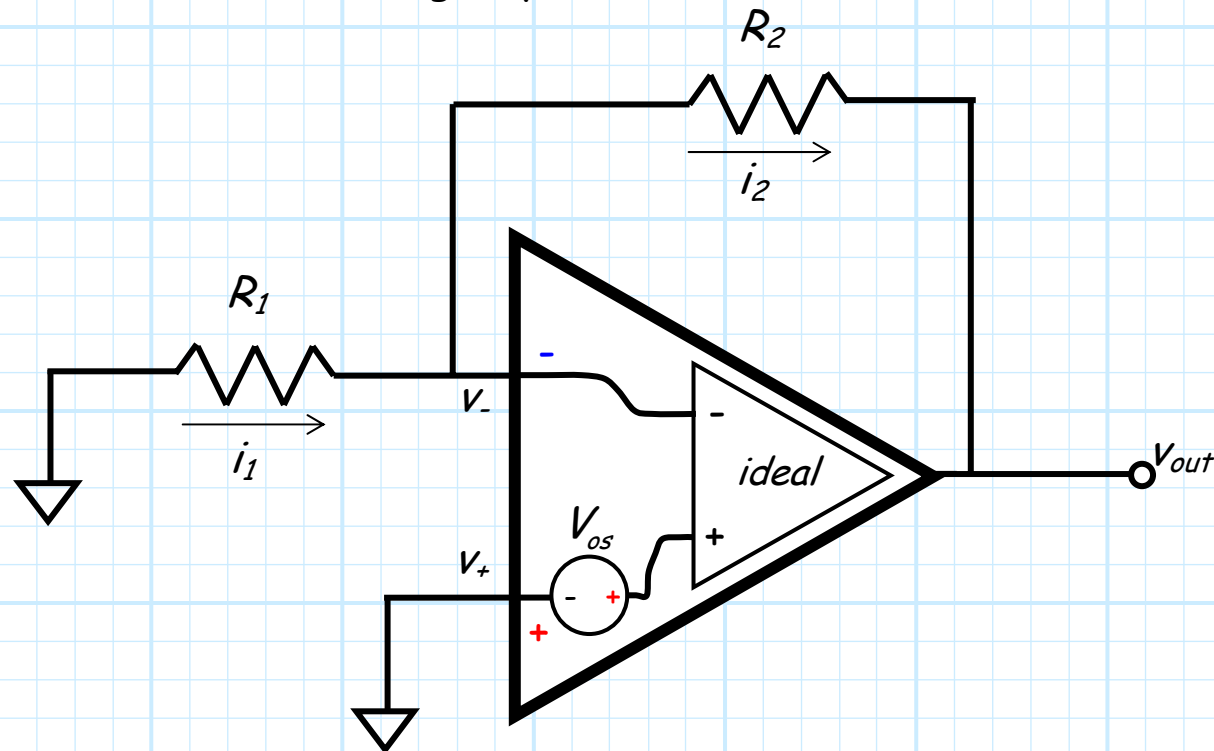
## It's the non-inverting amplifier!

Likewise, if we set the input voltage source to ground potential (i.e.,  $v_{in} = 0$ ), it is evident that we have a non-inverting amplifier:



And so the output voltage is:

$$v_{out} = \left( 1 + \frac{R_2}{R_1} \right) V_{os}$$

## Look at the DC offset!

The sum of these two results provides our previous answer:


$$v_{out} = -\left(\frac{R_2}{R_1}\right)v_{in} + \left(1 + \frac{R_2}{R_1}\right)V_{os}$$

Note the term:

$$\left(1 + \frac{R_2}{R_1}\right)V_{os}$$

is a **constant** with respect to  $v_{in}$ —its value does not change, **even** if the input voltage is zero!

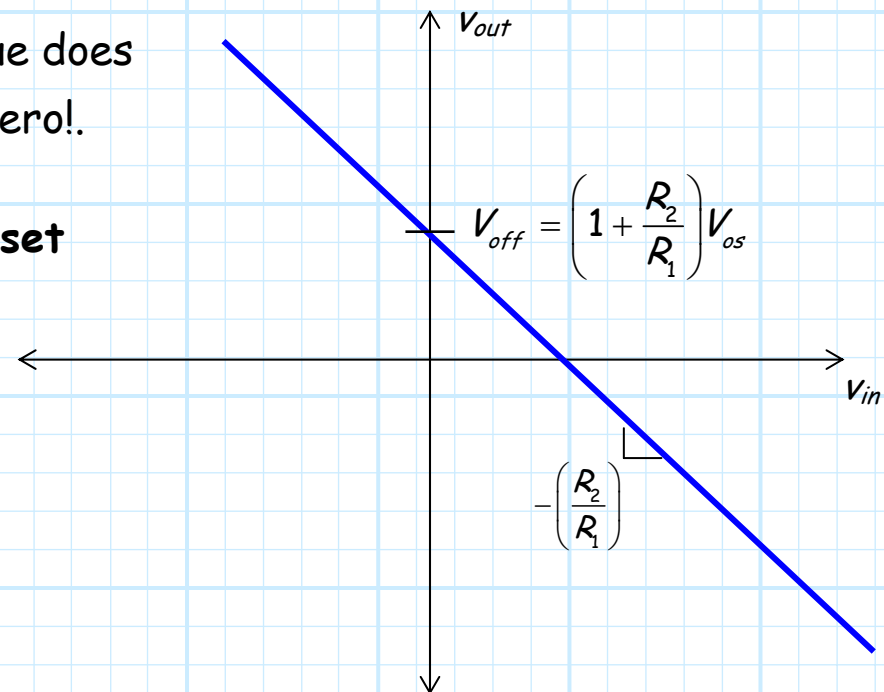Thus, the term represents an **output offset** voltage.



## How do we define gain?

**Q:** But what is the *gain* of this amplifier? The ratio  $v_{out}/v_{in}$  is not a constant!

$$\frac{v_{out}}{v_{in}} = -\left(\frac{R_2}{R_1}\right) + \left(1 + \frac{R_2}{R_1}\right) \frac{V_{os}}{v_{in}} \quad ????$$


**A:** Remember, it is more accurate and more general to define gain in terms of the **derivative**:

$$A_{vo} \doteq \frac{dv_{out}}{dv_{in}}$$

Which for this case provides the **same result** for the inverting amplifier:

$$A_{vo} = -\left(\frac{R_2}{R_1}\right)$$

# The Input Bias Current

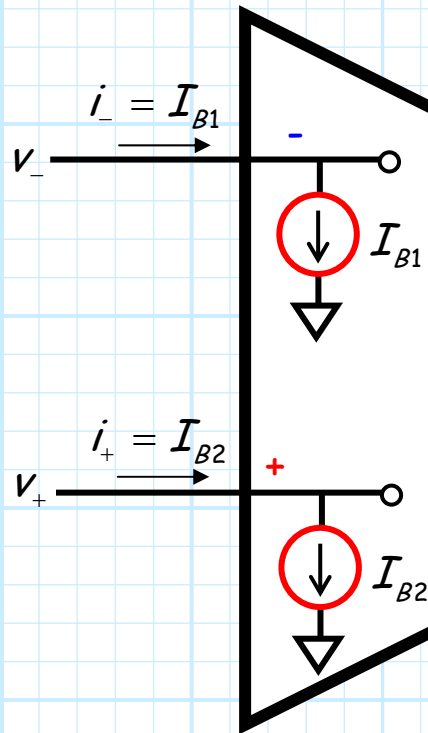

Real op-amps typically exhibit a phenomenon known as **input bias current**.

We find that there is a **small** amount of current flowing into each of the op-amp inputs (i.e.,  $i_- \neq 0$ , and  $i_+ \neq 0$ )!

These currents are **constant** currents—in other words, they are **independent** of the input terminal voltage

*Input Bias Current  
Op-Amp Model*

Real op-amps act like there are small **current sources** at the inputs!!!!!!

# The input offset current

The values of bias currents  $I_{B1}$  and  $I_{B2}$  are **approximately**—but **not exactly**—equal.

As a result, we typically express these currents in terms of their common-mode (i.e., average) and differential modes.

The common mode is called the Input **Bias** Current:

$$I_B = \frac{I_{B1} + I_{B2}}{2} \doteq \text{Input **Bias** Current}$$

The differential mode is called the Input **Offset** Current:

$$I_{os} = |I_{B1} - I_{B2}| \doteq \text{Input **Offset** Current}$$



## They seem so small, yet...

Thus, the two bias currents can be expressed as:

$$I_{B1} = I_B \pm \frac{I_{os}}{2} \qquad I_{B2} = I_B \mp \frac{I_{os}}{2}$$

**Typical** values of these parameters are, for example,  $I_B = 100\text{nA}$  and  $I_{os} = 10\text{nA}$ .

**Q:** *These bias current values are so tiny, we do we even care about them????*


**A:** Because they can cause **offset voltages** in op-amp circuits!

# Example: The Input Bias Current

**Q:** How do input bias currents  $I_{B1}$  and  $I_{B2}$  affect amplifier operation?

**A:** Consider both inverting and non-inverting configurations.

## Inverting Configuration

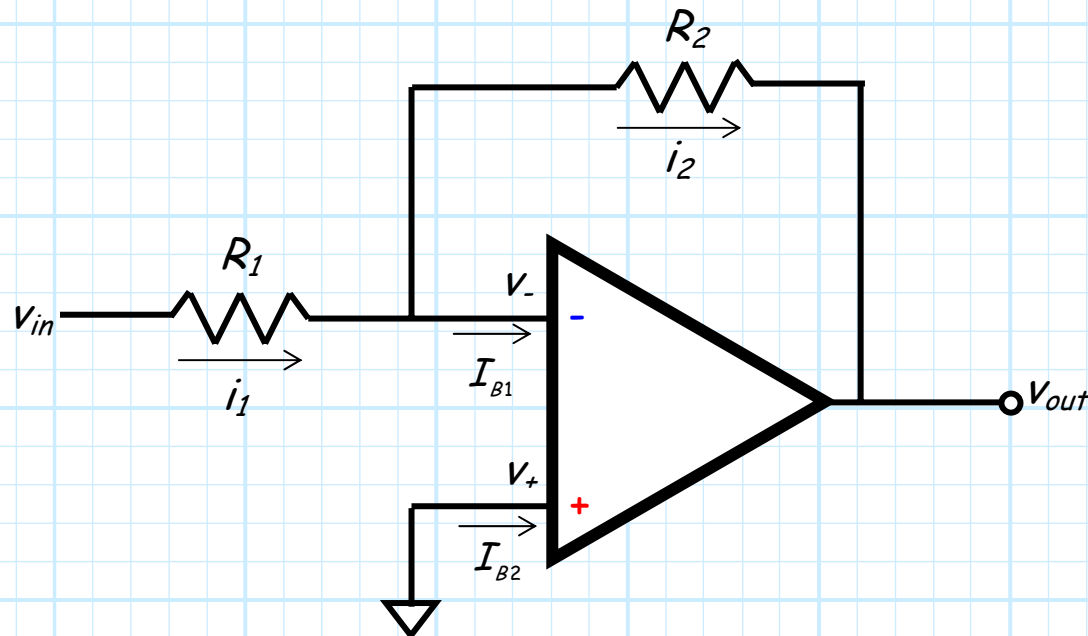

## KCL is now a bit more tricky!

In this case, we apply **KCL** and we find:

$$i_1 = i_2 + I_{B1}$$

However, we still find  $v_- \approx v_+ = 0$  (**neglecting** the input offset voltage) by virtue of the virtual short.

Therefore, from KVL and Ohm's Law:


$$i_1 = \frac{v_{in} - v_-}{R_1} = \frac{v_{in}}{R_1} \quad \text{and} \quad i_2 = \frac{v_- - v_{out}}{R_2} = \frac{-v_{out}}{R_2}$$

Combining these results:

$$\frac{v_{in}}{R_1} = \frac{-v_{out}}{R_2} + I_{B1}$$

The output voltage is thus:
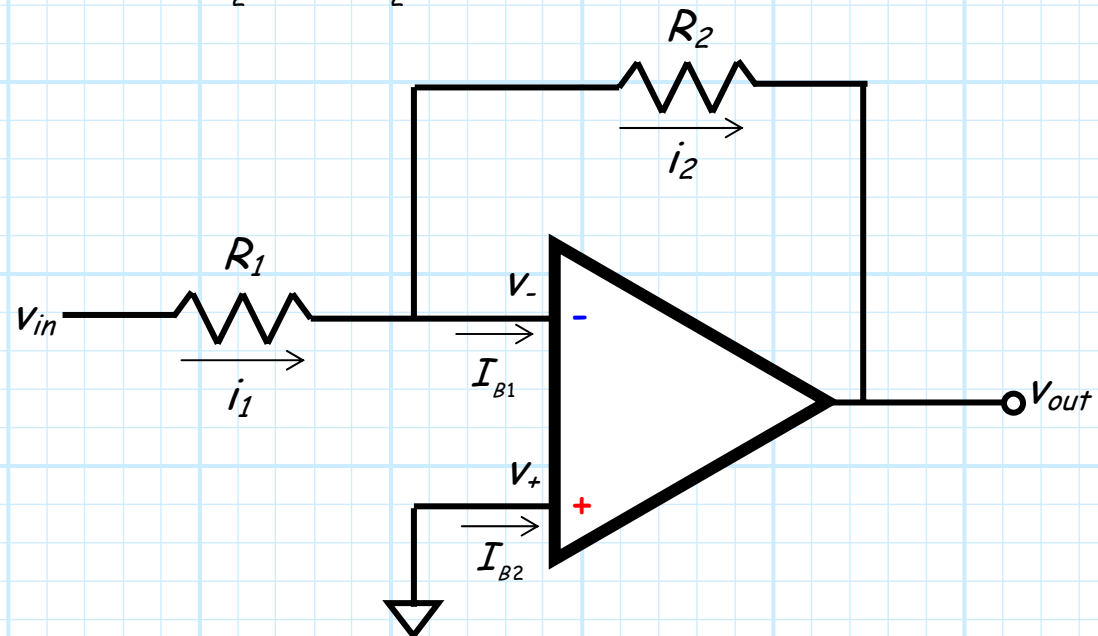
$$v_{out} = -\left(\frac{R_2}{R_1}\right)v_{in} + R_1 I_{B1}$$



## Should we make $R_1$ really small?

Note again that if  $I_{B1} = 0$ , the result reduces to the expected **inverting amplifier** equation:


$$V_{out} = -\left(\frac{R_2}{R_1}\right)V_{in}$$

The second term in the above expression ( $I_{B1} R_1$ ) therefore represents another **output offset voltage!**

It appears that we should keep the value of  $R_1$  **small** to minimize the output offset voltage.


**Q:** What would a small value of  $R_1$  do to the amplifier **input resistance**?

**A:**

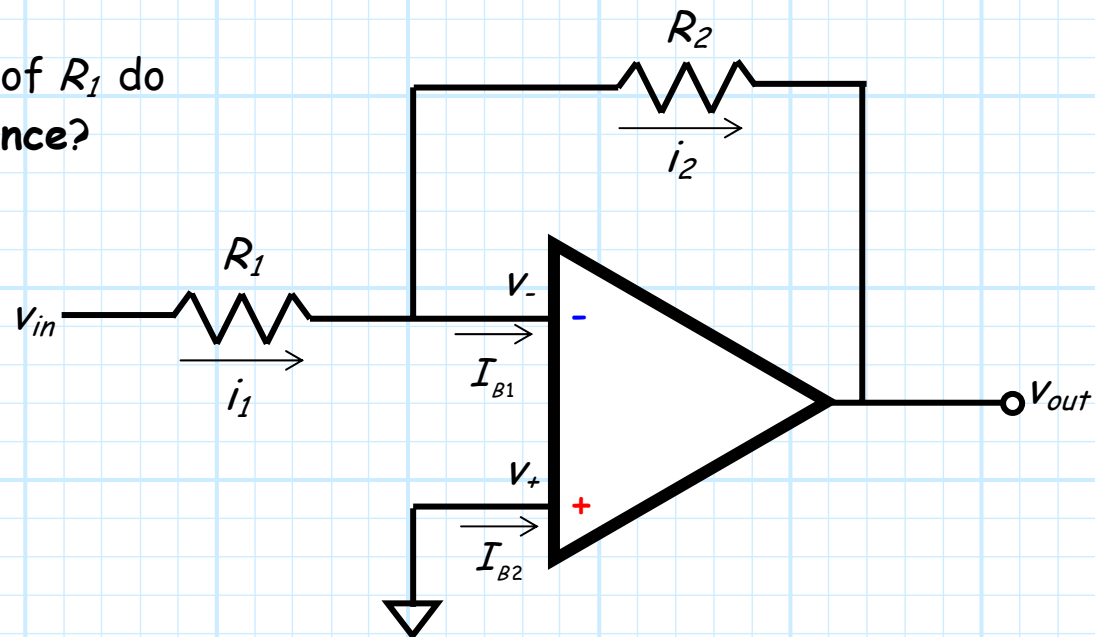

# Please welcome the non-inverting config.

## Non-Inverting Configuration

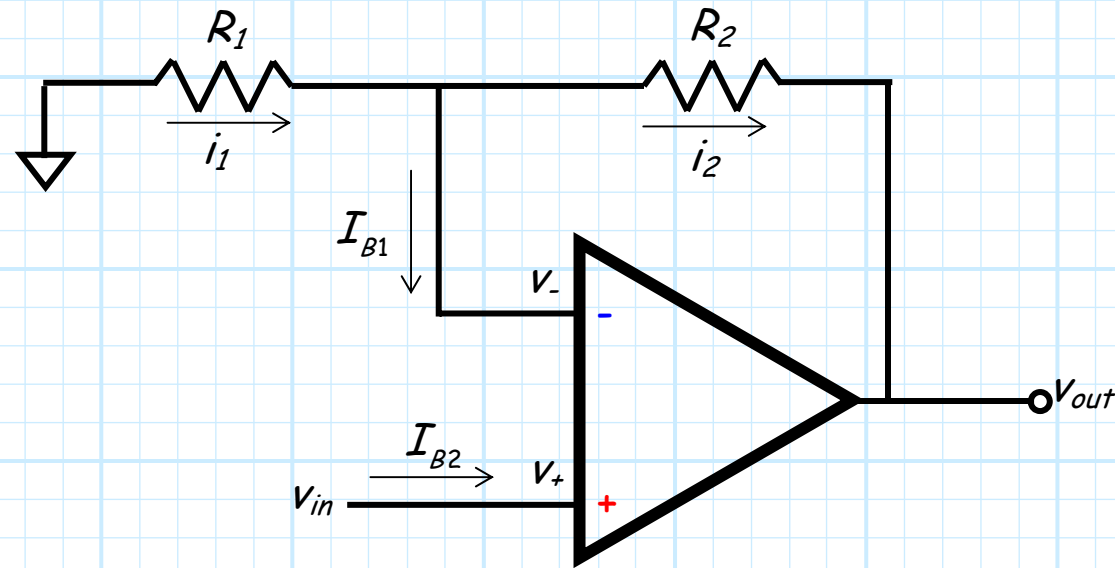

**Neglecting** the input offset voltage, we can use the **virtual short** to determine that:

$$V_- \approx V_{in}$$

and **KCL** provides the same result as that of the inverting amplifier:

$$i_1 = i_2 + I_{B1}$$

## Again, a DC output offset

From KVL and Ohm's Law:

$$i_1 = \frac{0 - v_-}{R_1} = \frac{-v_{in}}{R_1}$$

and likewise:


$$i_2 = \frac{v_- - v_{out}}{R_2} = \frac{v_{in} - v_{out}}{R_2}$$

Combining, we find:

$$\frac{-v_{in}}{R_1} = \frac{v_{in} - v_{out}}{R_2} + I_{B1}$$

or rearranging:
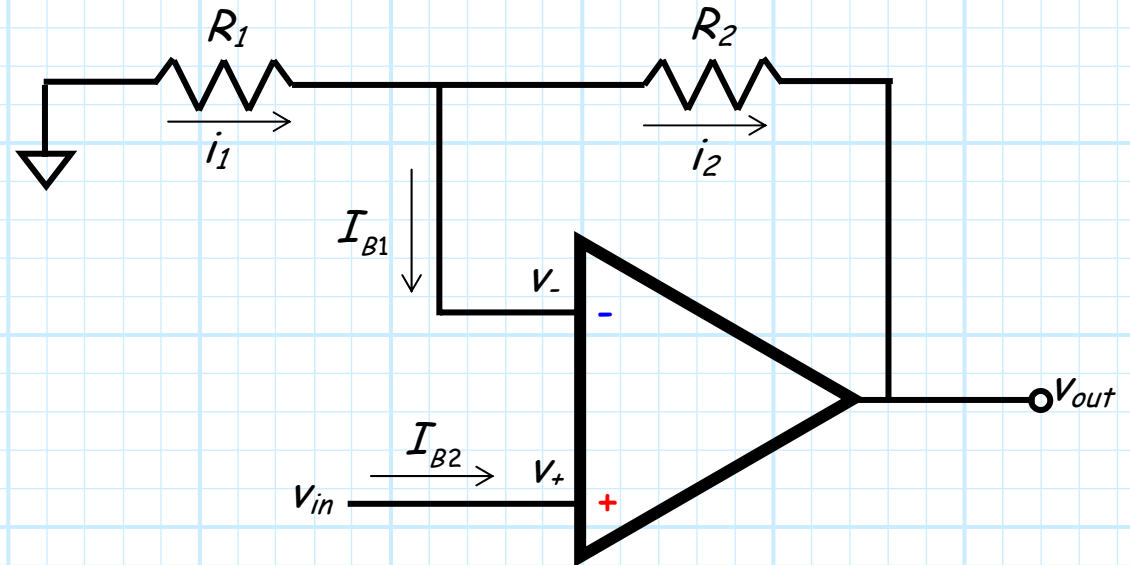
$$v_{out} = \left(1 + \frac{R_2}{R_1}\right) v_{in} + I_{B1} R_2$$



## We have another trick or two up our sleeve

Again, we find that this result is simply the ideal **non-inverting** expression:

$$V_{out} = \left( 1 + \frac{R_2}{R_1} \right) V_{in}$$

with an added **output offset voltage** term:

$$I_{B1} R_2$$

In this case, we find that this offset voltage is minimized by making feedback resistor  $R_2$  **small**.

In general, we find that the effects of the input bias currents can be minimized by using **small** resistor values.



However, we will find that there is an **additional strategy** for minimizing the effects of input bias currents!


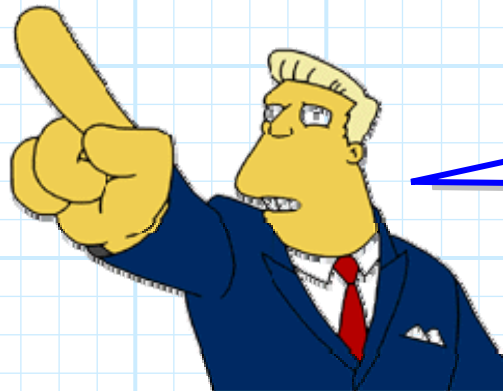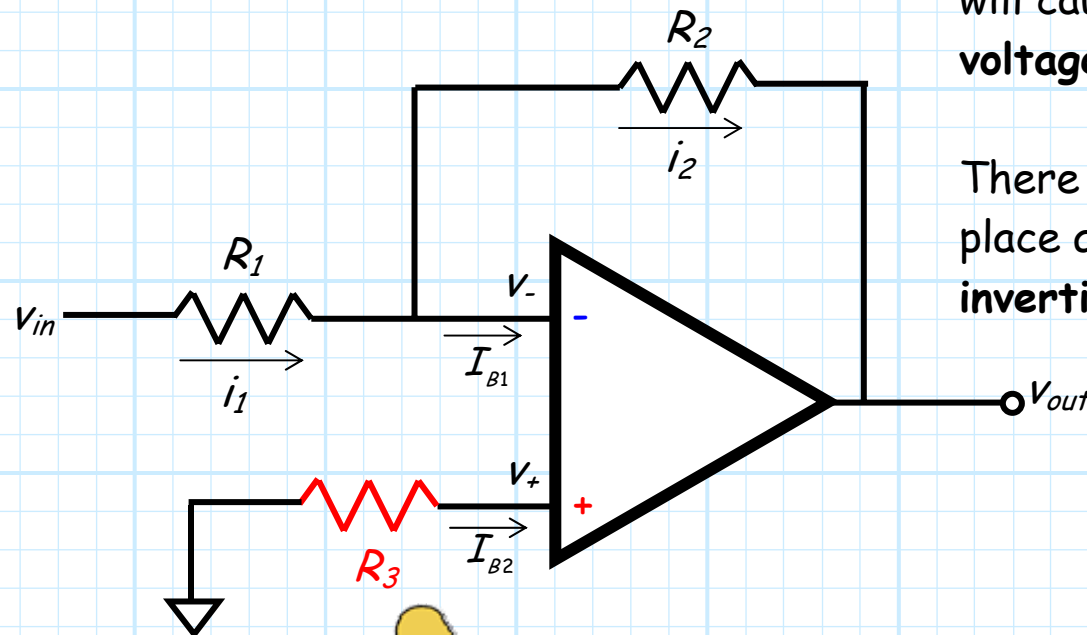
# Reducing the Effect of Input Bias Current

We found that the input bias current will cause an **offset** in the **output voltage**.

There is a **solution** to this problem—place a **resistor** ( $R_3$ ) on the **non-inverting input**!



**Q:** *Maria, why is this resistor here? I don't see how it can do any good.*



## The voltage $v_+$ is non-zero!

**A:** Let's **analyze** this circuit to determine how this new resistor helps.

First, notice that the voltage at the **non-inverting** terminal is now **non-zero!**

The bias current  $I_{B2}$  means that, by virtue of KVL:

$$v_+ = 0 - R_3 I_{B2} = -R_3 I_{B2}$$

Now, because of the **virtual short**:


$$v_- = v_+ = -R_3 I_{B2}$$

And from KCL:

$$i_1 = i_2 + I_{B1}$$

where from KCL and Ohm's Law:
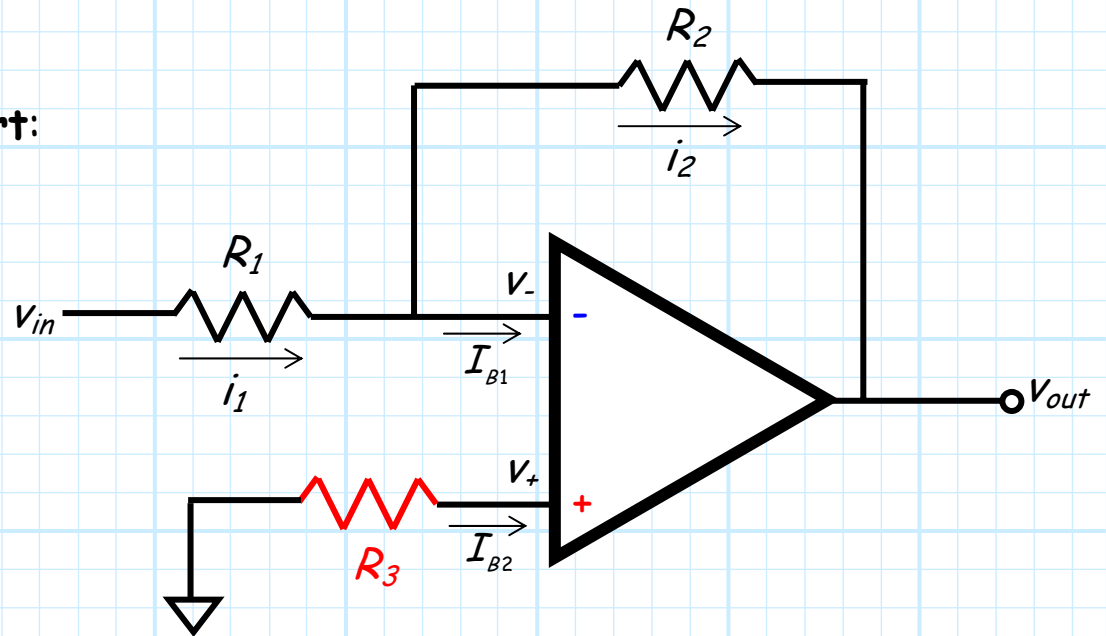
$$i_1 = \frac{v_{in} - v_-}{R_1} = \frac{v_{in} + R_3 I_{B2}}{R_1}$$




## It seems like this just made the offset even larger

And also from KCL and Ohm's Law:

$$i_2 = \frac{v_{in} - v_{out}}{R_2} = \frac{-(R_3 I_{B2} + v_{out})}{R_2}$$

Combining these results:
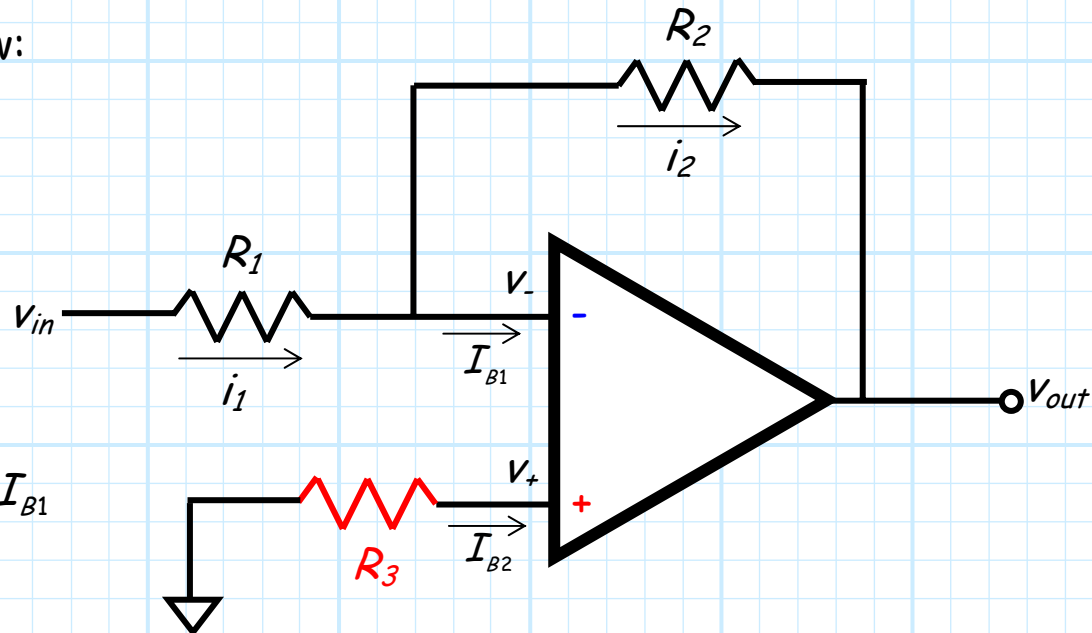
$$\frac{v_{in} + R_3 I_{B2}}{R_1} = \frac{-(R_3 I_{B2} + v_{out})}{R_2} + I_{B1}$$



Performing the usual algebraic gymnastics, we **rearrange** this result and find that the **output voltage** is:

$$v_{out} = \left( -\frac{R_2}{R_1} \right) v_{in} - \left( R_3 I_{B2} + \frac{R_2 R_3}{R_1} I_{B2} - R_2 I_{B1} \right)$$

## Awl be baak

Again we find the output consists of **two** terms. The first term is the **ideal** inverting amplifier result:

$$-\frac{R_2}{R_1} v_{in}$$

and the second is an output **D.C. offset**:



$$-(R_3 I_{B2} + \frac{R_2 R_3}{R_1} I_{B2} - R_2 I_{B1})$$

**Q:** Resistor  $R_3$  was supposed to **reduce** the D.C. offset, but it seems to have made things even **worse**. Fix this or I shall be forced to pummel you.

## We must choose the proper value of $R_3$ ...

**A:** Say we set the value of resistor  $R_3$  to equal  $R_3 = R_1 \parallel R_2$ , i.e.:

$$R_3 = \frac{R_1 R_2}{R_1 + R_2}$$

In this case, the **D.C. offset** becomes:

$$\begin{aligned} & - \left( \frac{R_1 R_2}{R_1 + R_2} I_{B2} + \frac{R_2^2}{R_1 + R_2} I_{B2} - R_2 I_{B1} \right) \\ & = - \left( \frac{(R_1 + R_2) R_2}{R_1 + R_2} I_{B2} - R_2 I_{B1} \right) \\ & = R_2 (I_{B1} - I_{B2}) \\ & = R_2 I_{os} \end{aligned}$$

Typically, the bias currents  $I_{B1}$  and  $I_{B2}$  are approximately equal, so that **offset current**  $I_{B1} - I_{B2} = I_{os}$  is very **tiny**.

Therefore, the resulting output **offset voltage** is likewise very **tiny!**




## ...and this is that proper value

Therefore, when designing an amplifier with **real** op-amps, **always** include a resistor  $R_3$  equal to the value:

$$R_3 = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

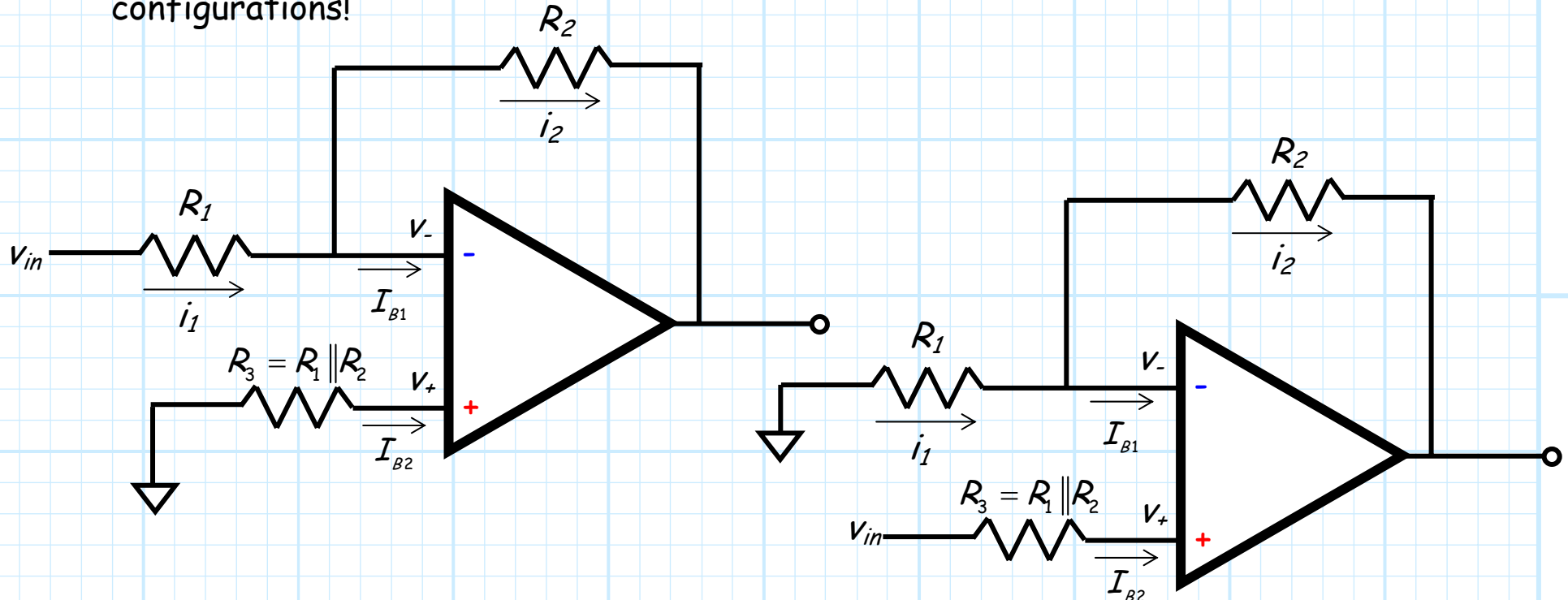This is true **regardless** of whether we use the **inverting** or **non-inverting** configurations!



## This is just the type of subtle point that shows up on an exam

If the impedances are **complex** (i.e.,  $Z_1(\omega)$  and  $Z_2(\omega)$ ), then set the resistor  $R_3$  based on the D.C. values of the impedances:

$$R_3 = Z_1(\omega = 0) \parallel Z_2(\omega = 0)$$

In other words, set the **capacitors** to **open** circuits and **inductors** to **short** circuits.

# Real Op-Amp Input and Output Resistances

The **input** resistances of real op-amps are **very large**, but of course **not** infinite!

Typical values of input resistances range from several hundred K Ohms to tens of **Mega** Ohms.

As a result, there is a **small** amount of current flowing into **input** terminals of a real op-amp.

**Q:** *Well of course! We just studied this topic.*

*We already know that there is a bias current  $I_B$  flowing into (or out of) real op-amp terminals!*



**A:** This is true! However, there is an **additional** amount of current flowing into the input terminals. This current is **not** a constant bias current, but instead is directly **proportional** to the input terminal voltage.


# The input resistance is large, but finite

Because the **input resistance** is finite, the **total current** into real op-amp terminals are:

$$i_+ = I_{B2} + \frac{v_+}{R_{in}}$$

$$i_- = I_{B1} + \frac{v_-}{R_{in}}$$

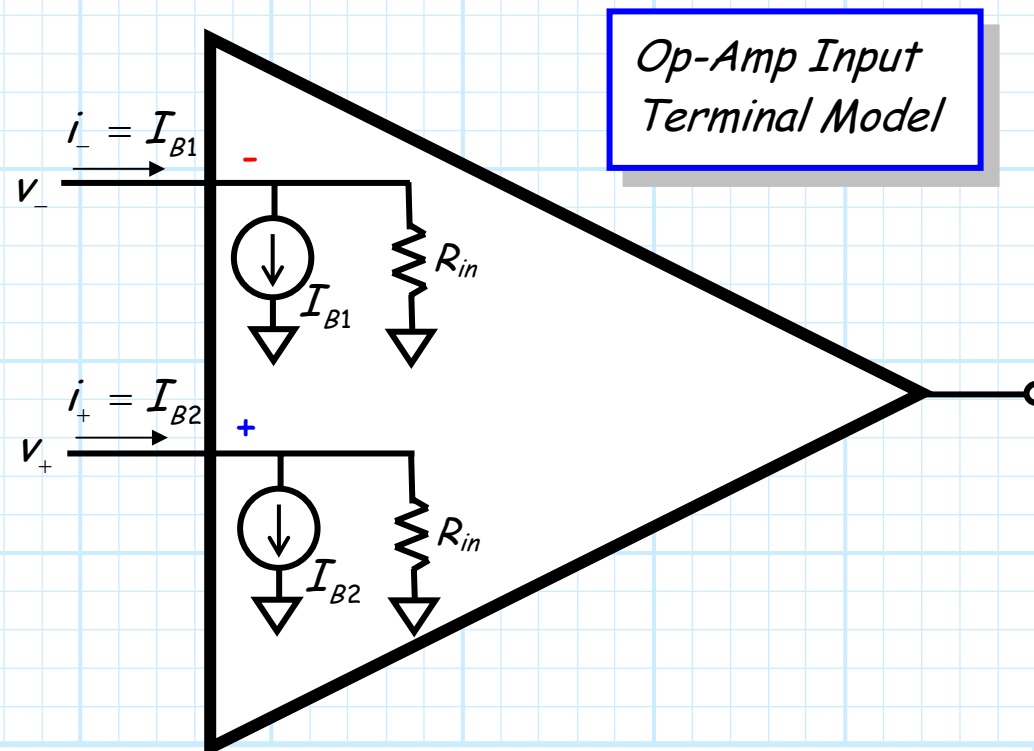As such, our input terminal **circuit model** is:





## Don't use resistors that are too large!

We find that the input current  $v_-/R_{in}$  or  $v_+/R_{in}$  will be **insignificant** (i.e., we can ignore its effect), provided that **all** other resistors used in an op-amp circuit are significantly **less** than the op-amp input resistance  $R_{in}$ .



**Q:** *But this would imply that we should never use resistor values greater than 100K in our op-amp circuits!*

**A:** That's **exactly** right!

If the resistor values that **you** use in your op-circuit design are of the order of  $R_{in}$ , you may find that **your** circuit behaves quite **differently** from what you expected!

## Worse even than finding haggis on the menu

Now let's examine the real values of op-amp **output** resistance.

**Instead** of the ideal value of zero, we find that the output resistances of real op-amps are **non-zero** (i.e.,  $R_{out}^{op} > 0$ )!

Recall that the output resistance of **both** the inverting and non-inverting configurations is approximately equal to the op-amp output resistance (i.e.,  $R_{out} = R_{out}^{op}$ ).

Thus, we find that the **output resistance** of real inverting and non-inverting amplifiers are likewise **non-zero**!




**Q:** *NO! The amplifier output resistance is not zero?!?*

*This means that the amplifier output will **not** be equal to the **open-circuit** voltage if a finite load is attached!*

**A:** This is absolutely correct!
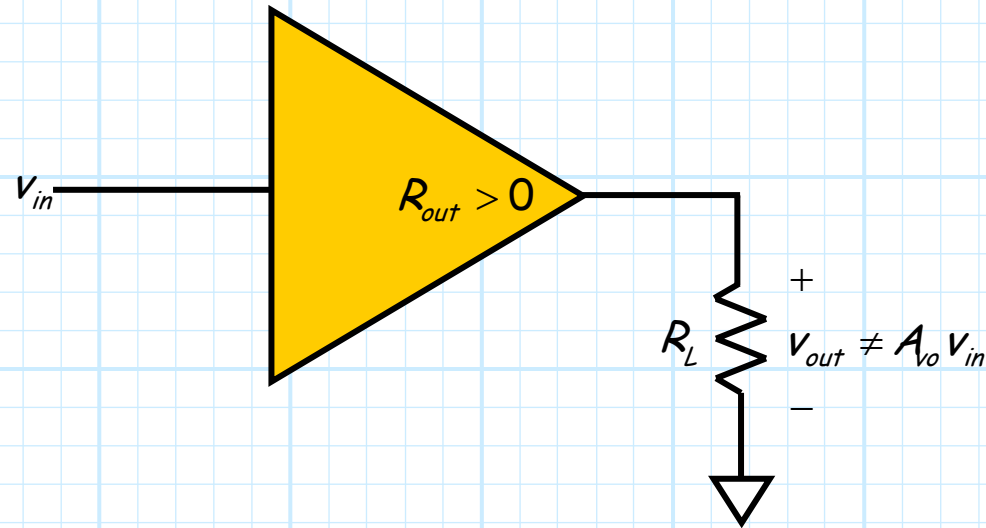
## Still, $R_{out}$ is usually pretty darn small

Remember, the output voltage of an amplifier is equal to the input voltage times the **open-circuit** voltage gain **only** when the amplifier output is connected to an **open circuit**.



But, recall that the output voltage will be **approximately equal** to the open-circuit voltage **if** the output resistance is much **smaller** than the load resistance. I.E.:

$$V_{out} \approx A_{vo} V_{in} \quad \text{if} \quad R_{out} \ll R_L$$

**Typical values of real op-amp output resistances are less than 5 Ohms!**