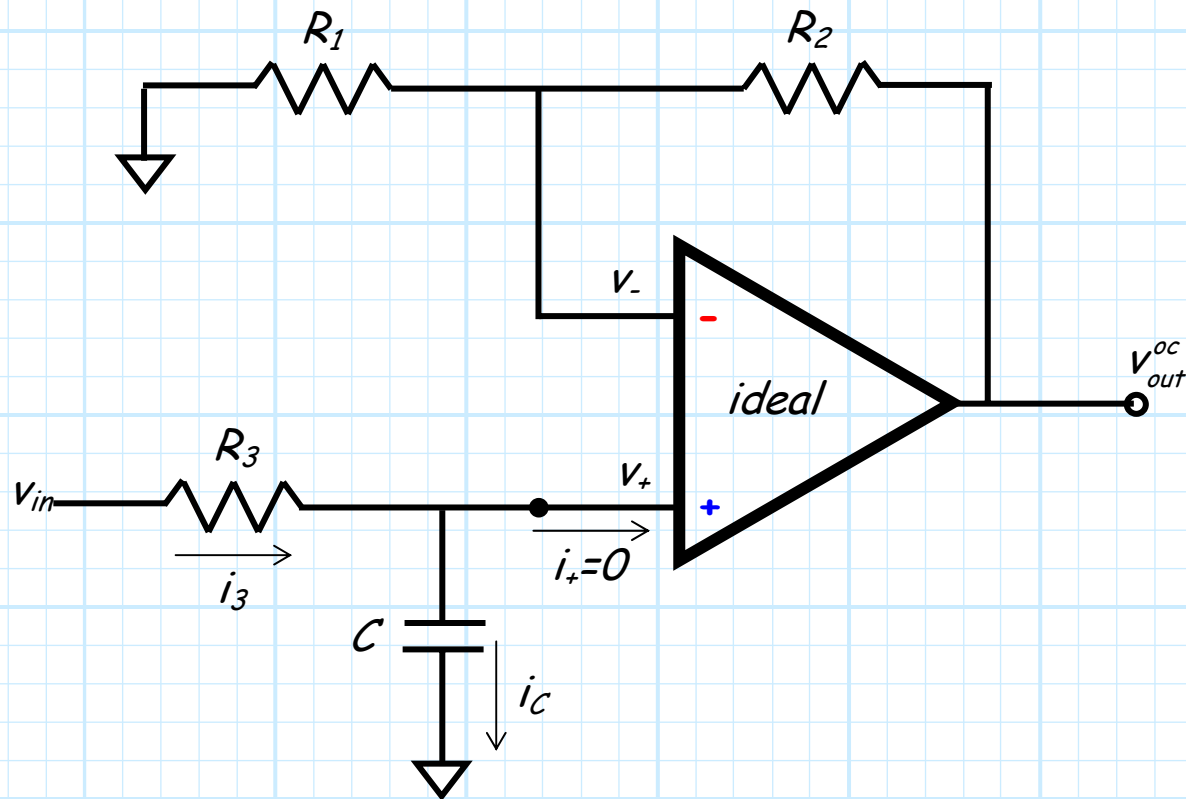


Example: A Non-Inverting Network

Let's determine the transfer function $G(\omega) = v_{out}^{oc}(\omega)/v_{in}(\omega)$ for the following circuit:



Some enjoyable circuit analysis

From KCL, we know:

$$i_3(\omega) = i_c(\omega) + i_+(\omega) = i_c(\omega) + 0 = i_c(\omega)$$

where:


$$i_3(\omega) = \frac{v_{in}(\omega) - v_+(\omega)}{R_3} \quad \text{and} \quad i_c(\omega) = \frac{v_+(\omega) - 0}{\left(\frac{1}{j\omega C}\right)} = j\omega C v_+(\omega)$$

Equating, we find an expression involving $v_{in}(\omega)$ and $v_2(\omega)$ only:

$$\frac{v_{in}(\omega) - v_+(\omega)}{R_3} = j\omega C v_+(\omega)$$

and performing a little algebra, we find:
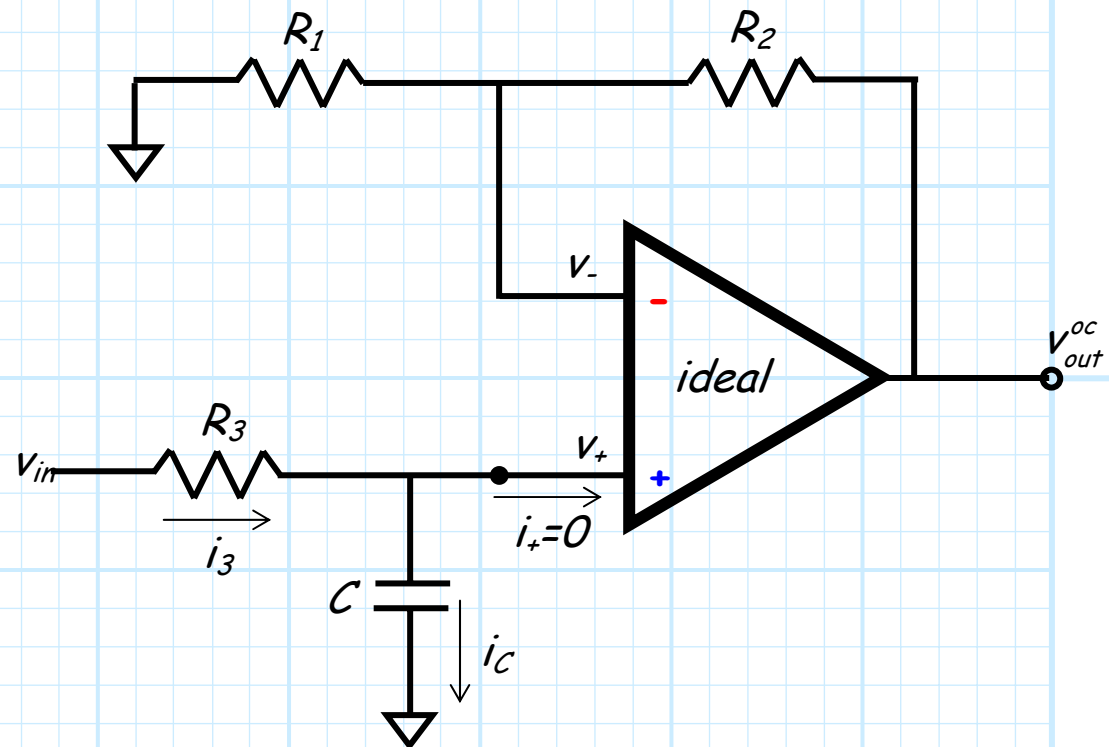
$$v_2(\omega) = \frac{v_{in}(\omega)}{1 + j\omega R_3 C}$$



No need to go further: we have a template!


The remainder of the circuit is simply the **non-inverting amplifier** that we studied earlier.

We know that:

$$v_{out}^{oc}(\omega) = \left(1 + \frac{R_2}{R_1}\right) v_+(\omega)$$

Combining these two relationships, we can determine the **complex transfer function** for this circuit:
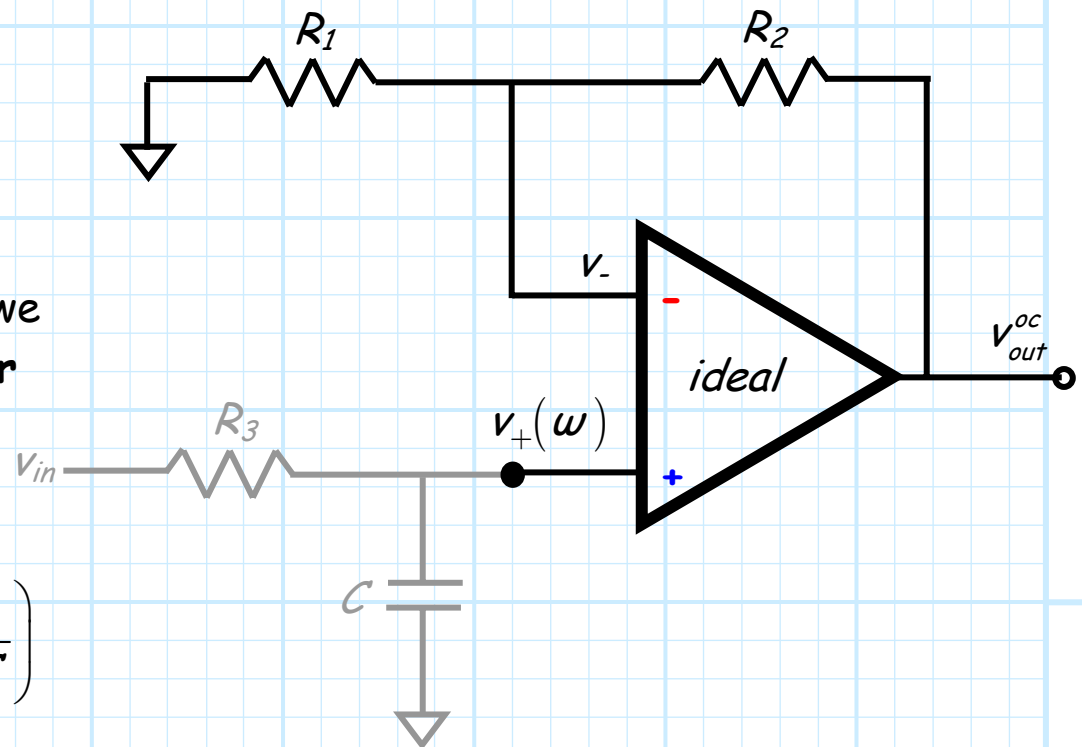
$$G(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{1}{1 + j\omega R_3 C}\right)$$



It's a low-pass filter!!

The **magnitude** of this transfer function is therefore:

$$|G(\omega)|^2 = \left(1 + \frac{R_2}{R_1}\right)^2 \frac{1}{1 + \left(\frac{\omega}{\omega_0}\right)^2}$$

where:

$$\omega_0 = \frac{1}{R_3 C}$$

This is a **low-pass filter**—one with **pass-band gain!**

